



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Seventh Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Jan. / Feb. - 2021

Analog CMOS VLSI Design


Time: 3 hrs

Max. Marks: 100


Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

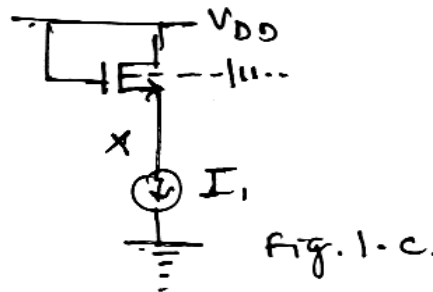- 1 a. Applying the principle of Electrostatic, derive an expression for the drain current equation of an NMOSFET. 8
- b. Discuss any two second order effects in MOSFET. 8
- c. Sketch g_m and g_{mb} of MOSFET M, in Fig. 1c as a function of the bias current - I 4



- 2 a. Draw the small signal model of a common source amplifier with diode connected load and derive an expression for its voltage gain. 8
- b. Using small signal model, derive an expression for the gain of a source follower. 8
- c. For the source follower in Fig. 2c, $(W/L)_1 = 20/0.5$, $I_1 = 200 \mu A$, $V_{TH0} = 0.5 V$, $2\phi_F = 0.6 V$, $\mu_n C_{ox} = 50 \mu A/V^2$, $\gamma = 0.33 V^{1/2}$. Compute V_{out} for $V_{in} = 1.4 V$ 4

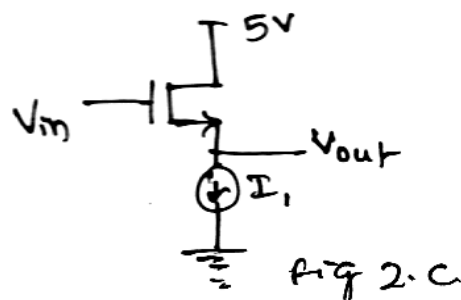

UNIT - II

- 3 a. Derive an expression for the voltage gain of a differential pair. 8
- b. Calculate the differential gain of the circuit in Fig. 3b. (Assuming $\lambda \neq 0$) 8

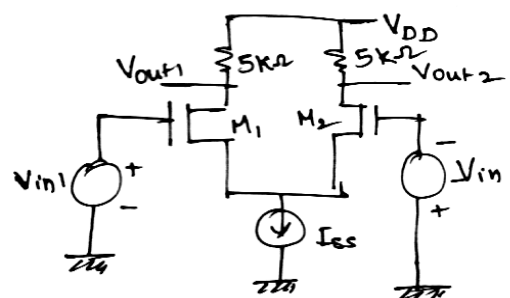


Fig. 3b

- c. Write a note on Gilbert cell. 4
- 4 a. Describe the operation of a basic current mirror circuit while stating their significance in analog circuits. 8
- b. Calculate the small signal voltage gain of the circuit in Fig. 4b.

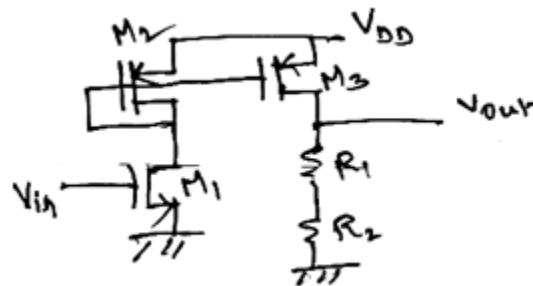


Fig. 4b

- c. State the significance of a cascode current mirrors, draw the schematic of a simple cascode current source. 4

UNIT - III

- 5 a. Discuss the performance parameters of Op-Amp, highlighting the trade off's. 10
- b. Draw the circuit diagram of two stage Op-Amp with cascoding and explain the functions of each stage. 10
- 6 a. With required schematics, describe the different gain boosting methods employed in Op-Amp's. 10
- b. With required schematics and equations describe the noise behavior in telescopic and folded cascode Op-Amp. 10

UNIT - IV

- 7 a. With required schematics and graph plots explain the operation of a two pole system. 10
- b. For the three stage ring oscillator show that $\omega_{osc} = \sqrt{3}\omega_0$ and $A_0 = 2$. 10
- 8 a. For Collpits oscillator, derive an expression for $\frac{V_{out}}{V_{in}}$ also show that;

$$\omega_R = \frac{1}{\sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}} \text{ and } g_m R_p = \frac{C_1}{C_2} \left(1 + \frac{C_2}{C_1} \right)^2$$
10

- b. Discuss the mathematical model of a voltage controlled oscillator, while stating the conditions of a harmonics. 10

UNIT - V

- 9 a. With required block diagram and waveforms, explain the operation of basic PLL. 10
- b. With required block diagram and waveforms, explain the operation of a charge pump PLL. 10
- 10 a. Write a note on non-ideal effects in PLL. 10
- b. Discuss the process of frequency synthesis and skew reduction. 10

