

U.S.N 

--	--	--	--	--	--	--	--	--	--

**P.E.S. College of Engineering, Mandya - 571 401***(An Autonomous Institution affiliated to VTU, Belagavi)***Seventh Semester, B.E. - Electrical and Electronics Engineering****Semester End Examination; Jan. / Feb. - 2021****Computer Techniques in Power Systems***Time: 3 hrs**Max. Marks: 100**Note: Answer FIVE full questions, selecting ONE full question from each unit.***UNIT - I**

1 a. Define the following with example:

i) Oriented graph

ii) Tree and co-tree

iii) Basic loop

10

iv) Basic cutset

v) Primitive network

b. For the power system shown in Fig. 1(b), obtain the incidence matrices  $a$ ,  $b$ ,  $c$  and  $k$  with ground as reference. Select a tree for which link elements are 1 – 2, 1 – 4, and 2 – 3. Verify the relation  $C_b = -B_l^t$ .

10

2 a. The bus incidence matrix is given below. Draw the oriented graph. Obtain augmented loop incidence matrix.

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & -1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & -1 \\ 0 & 1 & 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & 0 \end{bmatrix}$$

8

b. What is Primitive network? Obtain the performance equation in both admittance form impedance form.

6

c. Consider three passive elements whose data is given below. Form the primitive impedance matrix and primitive admittance matrix.

Element	Self impedance	Mutual impedance
1	j0.6	-
2	j0.5	j0.2 (with element1)
3	j0.7	-

6

**UNIT - II**3 a. Determine  $Y_{bus}$  by singular transformation for the system with as below:

Element No.	1	2	3	4	5
Bus code $p - q$	0 – 1	1 – 2	2 – 3	3 – 0	2 – 0
Self admittance	1.4	1.6	2.4	2.0	1.8

6

b. Derive an expression for the bus admittance matrix  $Y_{bus}$  using singular transformation method.

8

- c. The single line diagram of a four bus system is shown in Fig. 3(c). The data is given in the table. Formulate  $Y_{bus}$  without line 1 – 2. If line 1 – 2 is added, show how  $Y_{bus}$  is modified?

Line	$R$	$X$
1 – 2	0.05	0.15
1 – 3	0.1	0.3
2 – 3	0.15	0.45
2 – 4	0.1	0.3
3 – 4	0.05	0.15

6

- 4 a. Derive the expression for addition of a link to the partial network using building algorithm with no mutual coupling.
- b. Obtain  $Z_{bus}$  by building algorithm for the system shown in Fig. 4(b). All the impedances are in p.u. Add the elements in the order specified.

10

10

**UNIT - III**

- 5 a. Explain how buses are classified in a power system to perform load flow analysis?
- b. Obtain the voltage at bus 2 for the system shown in Fig. 5(b) using G-S method, if  $V_1 = 1\angle 0^\circ$  p.u .
- c. Compare the load flow methods with respect to storage requirements, computation time or iteration and number of iterations.
- 6 a. Derive the expression for the diagonal elements of sub matrices of the Jacobian in Newton Raphson method of load flow analysis.
- b. Obtain the voltages at all buses for three bus system shown in Fig. 6(b) at the end of first iteration by N-R method. The data is given in the table below,

6

8

6

8

Line data	$SB$	$EB$	$R(Pu)$	$X(Pu)$	$Bc/2$	
	1	2	0.0	0.1	0.0	
	1	3	0.0	0.2	0.0	
	2	3	0.0	0.2	0.0	
Bus data	$Bus\ no.$	$P_G$	$Q_G$	$P_D$	$Q_D$	$V_{sp}$
	1(slack)	-	-	-	-	1.0
	2(PV)	5.3217	-	-	-	1.1
	3(PQ)	-	-	3.6392	0.5339	-

12

**UNIT - IV**

- 7 a. Derive the necessary condition for economic operation of generators neglecting transmission losses.
- b. The fuel costs in Rs/hr for two plants are  $F_1 = 0.004 p_1^2 + 8p_1 + 10$ ;  $F_2 = 0.006 + P_2^2 + 9P_2 + 15$ .  
The system is operating on economic load dispatch with  $P_1 = P_2 = 500$  MW and  $\frac{\partial P_L}{\partial P_2} = 0.2$ .  
Find penalty factor of plant1.

6

6

- c. Obtain the expression for B coefficient considering two plant systems. 8
- 8 a. Compute the loss coefficients for the network shown in Fig. 8(a) using the given data; 8
- $I_a = (1.0 - j0.15)p.u.$   $Z_a = (0.02 + j0.15)p.u.$   
 $I_b = (0.5 - j0.1)p.u.$   $Z_b = (0.03 + j0.05)p.u.$   
 $I_c = (0.2 - j0.05)p.u.$   $Z_c = (0.02 + j0.25)p.u.$
- b. Explain the performance curves of thermal plant. 4
- c. The fuel cost of two generating plants are given below; 8
- $F_1 = 1.5 + 20P_{G1} + 0.1P_{G1}^2 \text{ Rs/h}$   $F_2 = 1.9 + 30P_{G2} + 0.1P_{G2}^2 \text{ Rs/h}$
- Find the optimal schedule for the demand  $P_D = 200 \text{ MW}$ . Also find the savings per day when they share the load equally.

**UNIT - V**

- 9 a. Explain with necessary condition the solution of swing equation by point- by-point method. 10
- b. With necessary equation, describe the solution of swing equation using modified Euler's method. 10
- 10 a. Explain with Phasor diagrams and necessary expression. The synchronous machine Models employed in transient stability studies. 10
- b. Describe the solution of swing equation using RK method. 10

