



U.S.N

## P.E.S. College of Engineering, Mandya - 571 401

*(An Autonomous Institution affiliated to VTU, Belagavi)*

**Third Semester, B.E. - Electronics and Communication Engineering**

**Semester End Examination; Dec. - 2019**

### Network Analysis and Synthesis

*Time: 3 hrs*

*Max. Marks: 100*

**Note:** i) PART - A is compulsory. **Two** marks for each question.

ii) PART - B: Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

Q. No.	Questions	Marks
	<b>I : PART - A</b>	<b>10</b>
I a.	State Norton's theorem.	2
b.	Define the following:	2
	i) Magnitude Scaling                    ii) Frequency Scaling	
c.	Find the Laplace transform of $t^2$ .	2
d.	Define planar graph. Give an example.	2
e.	Test whether the polynomial is Hurwitz or not give reason $P(s) = s^4 + 4s^3 + 3s + 2$	2


### II : PART - B

90
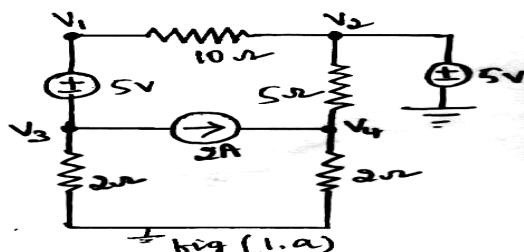
#### UNIT - I


18

- 1 a. For the network shown in Fig.1 (a), determine the node voltages  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$  using nodal analysis.




9

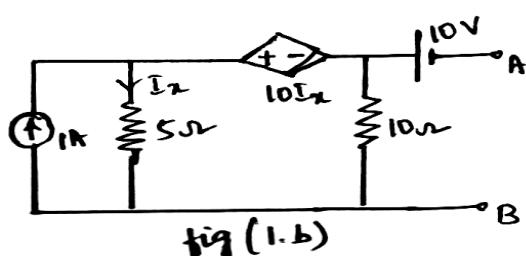- b. Find the Thevin's equivalent network shown in Fig.1 (b).



9

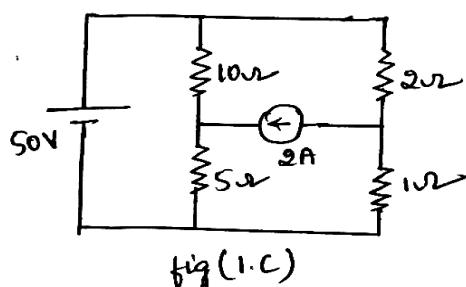- c. Determine the current in the  $5\Omega$  resistor of the network shown in Fig.1(c)



9


## UNIT - II

18

- 2 a. Define Q-factor and Prove that  $Q = \frac{1}{WRC}$ .


9

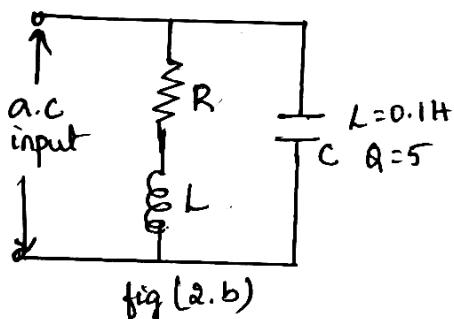- b. For the circuit shown in Fig. 2(b), determine the value of capacitance and coil resistance at resonant frequency of 500 rad/s and  $f_1$  and  $f_2$ .



9

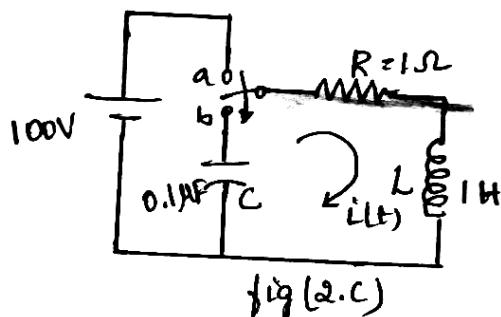- c. In the circuit shown in Fig. 2(c) the switch is moved from 'a' to 'b' at  $t = 0$ . Find the value of  $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ , at  $t = 0^+$ .



9

## UNIT - III

18

- 3 a. State and prove; i) Time Differentiation theorem      ii) Time Integration theorem.

9

- b. Find the Laplace transform of the following:

$$i) e^{-at} \cos wt \quad ii) f(t) = \begin{cases} (t+1) & 0 \leq t \leq 2 \\ 3 & t > 2 \end{cases} \quad iii) 5 + 4e^{-2t}$$

9

- c. Determine the Inverse Laplace transform of the following using Convolution method:


$$i) \frac{1}{(s-2)(s+2)^2} \quad ii) \frac{1}{(s+1)(s^2+1)}$$

9
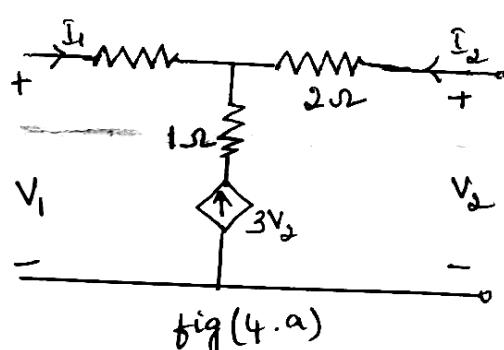
## UNIT - IV


18

- 4 a. Obtain Y-parameters for the network shown in Fig. 4(a).



9

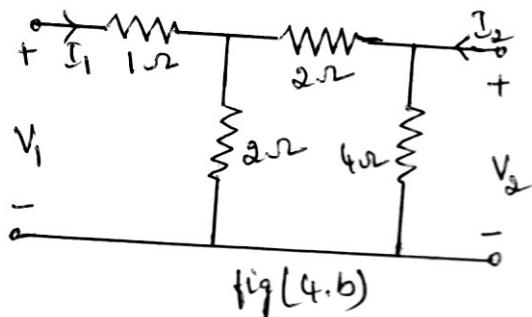- b. Determine hybrid parameters for the network of Fig. 4(b).



9

- c. The graph of a network is shown in Fig.4(c). Write the,

i) Incidence Matrix

ii) Tieset matrix

iii) Cutset matrix

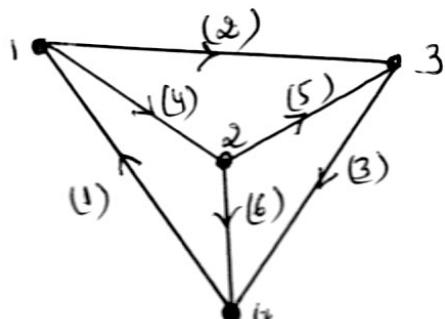


fig (4.c)

9

### UNIT - V

18

- 5 a. Define Hurwitz polynomial. Test whether the polynomial  $P(s) = s^5 + 3s^3 + 2s$  is Hurwitz.

9

- b. Test whether  $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$  is positive real function.

9

- c. Realize the Foster-I form of the following impedance function,

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

9

\* \* \*