



**P.E.S. College of Engineering, Mandya - 571 401**  
 (An Autonomous Institution affiliated to VTU, Belagavi)  
**Third Semester, B.E. – Information Science and Engineering**  
**Semester End Examination; Dec. - 2019**  
**Digital Design**

Time: 3 hrs

Max. Marks: 100

**Note:** I) **PART - A** is compulsory. One question for 2 marks from each unit.

II) **PART - B:** Answer any **two** sub questions (from a, b, c) for Maximum of 18 marks from each unit.

| Q. No.  | Questions   | Marks     |
|---|---|-----------|
| <b>I : PART - A</b>   |   | <b>10</b> |
| I a.  | Draw the logic circuit for the following equations :<br>i) $Y = \overline{A}BC + ABC$ ii) $Y = (\overline{A} + B + C)(A + B + \overline{C})$  | 2         |
| b.  | Convert the following BCD numbers into their decimal equivalents :<br>i) 100000010011      ii) 0111001001011001   | 2         |
| c.  | Distinguish between PLA versus PAL.   | 2         |
| d.  | Draw the circuit diagram and truth table of SR flip flops using NOR and NAND gates  | 2         |
| e.  | Write a state transition diagram of sequence detector in Moore and Mealy model.   | 2         |
| <b>II : PART - B</b>  |   | <b>90</b> |
| <b>UNIT - I</b>   |   | <b>18</b> |
| 1 a.  | Write each to the following min term Canonical formulas in algebraic form and construct their corresponding truth tables:<br>i) $f(x, y, z) = \sum m(0, 2, 4, 5, 7)$ ii) $f(w, x, y, z) = \sum m(1, 3, 7, 8, 9, 14, 15)$  | 9         |
| b.  | Write a Boolean expression for each of the logic diagram in Fig.1(b)  | 9         |
| <p align="center">(a)</p> <p align="center">(b)</p> <p align="center">(c)</p> <p align="center">Fig 1 (b)</p> |   |           |
| c.  | Using K-maps determine all the minimal sums and minimal products for each of the following Boolean functions.<br>i) $f(w, x, y, z) = \sum m(0, 1, 6, 7, 8, 14, 15)$<br>ii) $f(w, x, y, z) = \prod M(4, 6, 7, 8, 12, 14)$<br>iii) $f(w, x, y, z) = \overline{w}xz + xyz + w\overline{x}z + x\overline{y}z$ | 9         |

**UNIT - II**

**18**

- 2 a. Realize the function  $f(x, y, z) = \sum m(0, 2, 3, 5)$  using 4:1 line multiplexer. 9
- b. Write and explain the parity generator and checker circuits. 9
- c. Explain the construction of 4-bit carry lookahead adder. 9

**UNIT - III**

**18**

- 3 a. Realize the following Boolean expression using Programming Logic Array (PLA) and Programming Array Logic (PAL) : 9
  - i)  $f_1(w, x, y, z) = \sum m(2, 4, 5, 10, 12, 13, 14)$
  - ii)  $f_2(w, x, y, z) = \sum m(2, 9, 10, 11, 13, 14, 15)$
- b. What is the full scale output voltage of a 6 bit binary ladder of 0 = 0 V and 1 = +10 V of an 8-bit ladder? Find the output voltage of a 6-bit binary ladder with the following inputs? 9
  - i) 101001            ii) 111011            iii) 110001
- c. Explain the Read Only Memory diode circuits. 9

**UNIT - IV**


**18**

- 4 a. Give the characteristic equation, excitation table, state diagram of SR flip flop and JK flip flop. 9
- b. Illustrate how JK flip flops can be converted to SR flip flops? 9
- c. With circuit diagram, explain serial in serial out and parallel in serial out shift registers. 9

**UNIT - V**

 **18**

- 5 a. Design an asynchronous up down counter. 9
- b. Using row elimination method to reduce the state diagram as shown in Fig. 5(b). 9



- c. i) Analyze the mealy model asynchronous sequential circuit of Fig. 5(c) and show its stable state and corresponding outputs. 9
- ii) Give the state diagram of the circuit as shown in Fig.5(c)

