



# P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

First Semester, B.E. - Semester End Examination; April - 2021

**Basic Electronics**  
(Common to all Branches)

Time: 3 hrs

Max. Marks: 100

### Course Outcomes

The Students will be able to:

CO1: Apply knowledge of physics and mathematics to understand operation of PN diodes, Zener diodes MOSFET, solar cells, LCD, CRT, Transducers, modulation techniques and Opamps.

CO2: Analyze circuits built with diodes, Zener diodes, MOSFET and Opamp.

CO3: Design simple circuit to perform rectification, voltage regulation, Opamp based amplifier, summer and filter, MOSFET based amplifier, digital circuit.


CO4: Analyze and implement basic Digital Electronic circuits for a given application using knowledge of Boolean Algebra and Basic gates.

CO5: Discuss different modulation techniques and communication systems.

**Note: I) PART - A** is compulsory. **Two** marks for each question.

**II) PART - B:** Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

Q. No.	Questions	Marks	BLs	COs	POs
<b>I : PART - A</b>		<b>10</b>			
I a.	Draw the block diagram of power supply unit.	2	L1	CO1	PO1
b.	List any two differences between Deflection type and Enhancement type MOSFET.	2	L1	CO1	PO1
c.	List the ideal characteristics of Op-Amp.	2	L1	CO1	PO1
d.	Obtain 1's and 2's complement of $(011010)_2$ .	2	L1	CO4	PO2
e.	Differentiate the characteristics between Amplitude Modulation (AM) and Frequency Modulation (FM).	2	L1	CO1	PO1
<b>II : PART - B</b>		<b>90</b>			
<b>UNIT - I</b>		<b>18</b>			
1 a.	With necessary circuit diagram and wave forms, explain center tapped full wave rectifier.	9	L3	CO2	PO2
b.	Define Voltage regulation. Analyze the working of Zener diode as voltage regulator with fixed $V_i$ and variable $R_L$ .	9	L3	CO2	PO2
c.	Define Load line. Determine $I_{DQ}$ and $V_{DQ}$ for the network shown in Fig.1(c).	9	L2	CO3	PO2

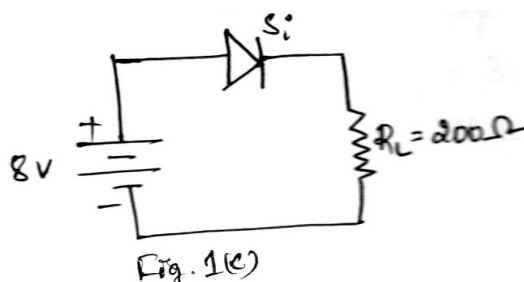


Contd...2

**UNIT - II**

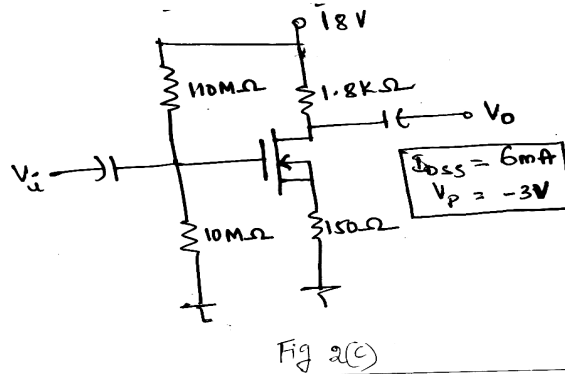**18**

- 2 a. Describe the operation and characteristics of *n*-channel deflection type MOSFET with necessary diagram and equation. 9 L2 CO2 PO2
- b. Explain the construction, operation of CMOS. Also illustrate the working of CMOS inverter. 9 L2 CO2 PO2
- c. Determine the following for the network in the Fig.2(c):
  - i)  $V_{GSQ}$
  - ii)  $I_{DQ}$
  - iii)  $V_{DS}$



9 L2 CO3 PO2

**UNIT - III**

**18**

- 3 a. Determine the output voltage of an Op-Amp for input voltage of  $V_{i1} = 350 \mu V$  and  $V_{i2} = 200 \mu V$ . The amplifier has a differential gain of  $A_d = 4000$  and the value of CMRR is i) 1000 and ii)  $10^6$ , conclude by comparing the results. 9 L3 CO2 PO2
- b. Explain the Op-amp with necessary circuit diagram and equations for the following:
  - i) 2-input inverting summing amplifier
  - ii) Integrator9 L2 CO3 PO2
- c. Derive the expression for the output voltage and gain of an inverting Op-Amp with neat circuit diagram and equivalent diagram. 9 L4 CO4 PO2

**UNIT - IV**

**18**

- 4 a. Design and implement the full adder using 2 half adders with characteristics equation for sum and carry. 9 L4 CO4 PO2
- b. Compute the following :
  - i)  $(1234.12)_{10} = ( )_2 = ( )_8 = ( )_{16}$
  - ii)  $(1010101) \times (010111)$
  - iii) Perform binary subtraction using 2's complement  $(15)_{10} - (03)_{10}$9 L2 CO4 PO2
- c. Implement the following logic gates using only NAND and NOR:
  - i) AND
  - ii) OR
  - iii) XOR9 L2 CO4 PO2

**UNIT - V****18**

- |      |  |          |    |     |     |
|------|--|----------|----|-----|-----|
| 5 a. | Explain super hetero dyne receiver used in radio receivers with neat diagram.                          | <b>9</b> | L2 | CO5 | PO2 |
| b.   | Write a short note on;   |          |    |     |     |
|      | i) Resistive transducer  | <b>9</b> | L2 | CO5 | PO2 |
|      | ii) Capacitive transducer  |          |    |     |     |
| c.   | Explain Amplitude Modulation (AM) with wave forms and equation along with spectrum diagram of AM wave. | <b>9</b> | L2 | CO1 | PO1 |

**\* \* \***