



P.E.S. College of Engineering, Mandya - 571 401
(An Autonomous Institution affiliated to VTU, Belagavi)
Third Semester, B.E. - Electronics and Communication Engineering
Semester End Examination; March - 2021
Analog Electronic Circuits

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1 - **Apply** the knowledge of physics to describe the operation and characteristics of Op-Amps.CO2 - **Discuss** the working of op-amp applications, signal generators, voltage regulators, ADC, DAC and PLL.CO3 - **Analyze** the frequency response, stability and applications of op-amps.CO4 - **Design** the different op-amp applications circuits, signal generators, voltage regulators, ADC, DAC for a given specifications.CO5 - **Work** as individual or in groups to model different op-amp circuits using simulation tools.**Note:** I) **PART - A** is compulsory. **Two** marks for each question.II) **PART - B:** Answer any **Two** sub questions (from a, b, c) for Maximum of **18** marks from each unit.

Q. No.	Questions	Marks	BLs	COs	POs
I : PART - A		10			
I a.	Define PSRR.	2	L1	CO1	PO1
b.	Mention the frequency compensation methods.	2	L1	CO1	PO1
c.	Draw the circuit diagram of negative precision rectifier.	2	L1	CO1	PO1
d.	What should be the value of gain and the total phase shift around a loop of RC phase shift oscillator circuit?	2	L1	CO2	PO2
e.	Define lock range and capture range related PLL.	2	L1	CO1	PO1
II : PART - B		90			
UNIT - I		18			
1 a.	Design op-amp non-inverting amplifier with a voltage gain of 50 to produce an output voltage of 2 V.	9	L3	CO3	PO3
b.	With a circuit and design steps, explain the operation of high input impedance capacitor coupled voltage follower.	9	L2	CO2	PO2
c.	Sketch an op-amp circuit to output inverted amplified sum of two input voltages. Design this circuit to give sum of the two inputs which each ranges from 0.5 V to 1 V and the gain of the circuit is 2.	9	L2	CO2	PO2
UNIT - II		18			
2 a.	Describe the concept of frequency compensation and with a neat diagram, explain how compensation is provided internally?	9	L2	CO2	PO2
b.	Sketch the circuit of precision voltage source with Zener diode and design it to provide the output of 12 V. The available supply is ± 15 V. Provide the arrangement for $\pm 5\%$ tolerance of Zener diode voltage.	9	L2	CO3	PO3
c.	With a neat circuit diagram, explain the operation of inverting Schmitt trigger. Using 741 op-amp with a supply voltage of ± 12 V, design a inverting Schmitt trigger circuit to have trigger points of UTP = 0 V and LTP = -1 V.	9	L3	CO4	PO3

UNIT - III**18**

- 3 a. With a neat circuit, explain the working of full wave precision rectifier with input and output wave forms and with necessary equations. 9 L2 CO2 PO2
- b. Explain the operation of sample and hold circuit and discuss its performance parameters. 9 L2 CO2 PO2
- c. Explain operation of 555 Timer as an astable multivibrator. Design an astable multivibrator using 555 timer IC to generate a symmetrical square wave of 2 kHz with 50% duty cycle, assuming $C = 0.1 \mu\text{F}$. 9 L3 CO3 PO3

UNIT - IV**18**

- 4 a. With a neat sketch, explain the operation in Triangular / Rectangular wave generator circuit and write the expressions for;
- i) Peak to Peak amplitude of the Triangular wave 9 L2 CO2 PO2
- ii) The time taken by the output to swing from $-V_{\text{ramp}}$ to $+V_{\text{ramp}}$
- iii) Frequency of oscillation
- b. Sketch feedback network in RC phase shift oscillator and discuss its significance. Design phase shift oscillator to have output frequency of 500 Hz. Use $\pm 12 \text{ V}$ supply. 9 L2 CO3 PO3
- c. Explain the operation of adjustable output regulator and design this circuit for the following specifications: 9 L2 CO3 PO3
- $V_i = (18 \pm 3) \text{ V}$, $V_o = 9 \text{ V}$ at $I_o = 10 \text{ to } 50 \text{ mA}$; Zener Voltage, $V_Z = 5.6 \text{ V}$ and $I_{Z(\text{min})} = 5 \text{ mA}$.

UNIT - V**18**

- 5 a. Write an expression for the output voltage of inverted R / 2R ladder D / A converter. Explain its operation and also mention the advantages of this DAC. 9 L2 CO2 PO2
- b. With a neat diagram, waveform and analysis, explain the operation of dual slope, integrator ADC. Also mention its advantages and disadvantages. 9 L2 CO2 PO2
- c. Explain the operation of basic PLL system with block diagram and waveforms. 9 L2 CO2 PO2

* * *