



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
Third Semester, B.E. - Electronics and Communication Engineering
Semester End Examination; March - 2021
Digital Electronic Circuits

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1: Ability to apply the knowledge of mathematics and science to understand the operation of logic circuits and performance parameters.

CO2: Ability to apply the simplification techniques/methods to optimize and implement the digital functions/circuits.

CO3: Ability to analyze the given logic circuit based on the knowledge of digital elements.

CO4: Ability to design a combinational and sequential logic circuit for the given requirements/specifications.

CO5: Ability to understand and design the State machines with state graphs for sequential design.

Note: I) PART - A is compulsory. Two marks for each question.**II) PART - B: Answer any Two sub questions (from a, b, c) for Maximum of 18 marks from each unit.**

Q. No.	Questions	Marks	BLs	COs	POs
I : PART - A		10			
I a.	List the two bit maxterms.	2	L3	CO1	PO1
b.	Assuming ideal conditions design a D-flip flop using multiplexer.	2	L3	CO4	PO3
c.	Draw the schematic of a gated SR latch.	2	L2	CO4	PO3
d.	Compute the maximum number of flip-flops required to count five events.	2	L3	CO5	PO1
e.	Draw the schematic of a general Mealy machine.	2	L2	CO3	PO2
II : PART - B		90			
UNIT - I		18			
1 a.	Simplify the expression using K-map;				
	i) $f(A, B, C, D) = \sum m(0, 2, 4, 6, 9, 11, 13, 15)$	9	L3	CO2	PO2
	ii) $(a, b, c, d) = \overline{ab} + cd + ac + \overline{bc}$				
b.	Simplify the following Boolean expression using Quine-McCluskey method: $f(P, Q, R, S) = \sum m(1, 6, 8, 9, 10, 11, 14,) + \sum d(7, 13)$	9	L3	CO2	PO2
c.	Simplify the following expression using VEM technique:				
	i) $f(A, B, C, D) = \sum m(0, 2, 4, 5, 7, 9, 11, 13)$	9	L3	CO2	PO2
	ii) $f(A, B, C) = \prod m(0, 3, 5, 6, 7)$				
UNIT - II		18			
2 a.	Design a combinational circuit to add 2-bit gray code number A and B.	9	L4	CO4	PO3
b.	Design and implement 2-bit binary to gray code converter, using optimum configuration multiplexers.	9	L4	CO4	PO3

Contd... 2

- c. Illustrate the concept of combinational logic implementation using ROM and PLA.

9 L4 CO4 PO3

UNIT - III

18

- 3 a. With required transition table and characteristic equation, analyze the operation of SR flip flop.
- b. With required timing diagram, discuss the reasons of race around condition in JK flip flop, while illustrating / highlighting the possible solutions.
- c. Convert; i) D flip flop to JK flip flop and ii) T flip flop to D flip flop

9 L2 CO3 PO2

9 L3 CO3 PO2

9 L3 CO3 PO2

UNIT - IV

18

- 4 a. Design a sequential logic circuit to generate sequence $\{8 \rightarrow 4 \rightarrow 2 \rightarrow 1\}$ assuming appropriate initial condition.
- b. Design a sequential logic circuit to generate all the possible factors of factorial 8 (8!).
- c. Design an arithmetic circuit with two select lines S_1 and S_0 to generate the arithmetic operations as listed in Table. 4. c, draw the logic diagram.

9 L4 CO4 PO1

9 L4 CO4 PO1

S_1	S_0	$C_{in} = 0$	$C_{in} = 1$
1	1	$F = A$	$F = A + 1$
0	0	$F = A + B$	$F = A + B + 1$
1	0	$F = A + \bar{B}$	$F = A + \bar{B} + 1$
0	1	$F = A - 1$	$F = A$

9 L4 CO4 PO1

Table 4.c

UNIT - V

18

- 5 a. For the logic diagram given in Fig. 5(a),
 - i) Write the excitation table and derive the output equations
 - ii) Write the next state equations
 - iii) Construct / write transition table
 - iv) Draw the state diagram

9 L4 CO5 PO1

 


Fig. 5(a)

- b. Design a logic circuit to detect the sequence 1101(Use D flip flops).
- c. Discuss the concepts of Moore and Mealy machines while accounting the instances of their suitability.

9 L4 CO5 PO1

9 L3 CO5 PO1