



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
Third Semester, B.E. - Electronics and Communication Engineering
Semester End Examination; March - 2021
Network Analysis and Synthesis

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:


- CO1: Ability to apply the fundamental concepts in solving and analyzing different Electrical networks.
- CO2: Ability to solve circuits using appropriate technique.
- CO3: Ability to apply mathematics in analyzing and synthesizing the networks in time and frequency domain.
- CO4: Ability to analyze the performance of a particular network.
- CO5: Ability to formulate various synthesis methods for different one-port networks.

Note: I) PART - A is compulsory. Two marks for each question.

II) PART - B: Answer any Two sub questions (from a, b, c) for Maximum of 18 marks from each unit.


Q. No.	Questions	Marks	BLs	COs	POs
I : PART - A		10			
I a.	State superposition theorem applied to AC circuits.	2	L1	CO1	PO1
b.	Define quality factor and bandwidth of a series RLC circuits.	2	L1	CO1	PO1
c.	State initial value theorem.	2	L1	CO1	PO1
d.	Define two port network with an example.	2	L1	CO1	PO1
e.	Mention the properties of realization of RC functions.	2	L1	CO1	PO1
II : PART - B		90			
UNIT - I		18			

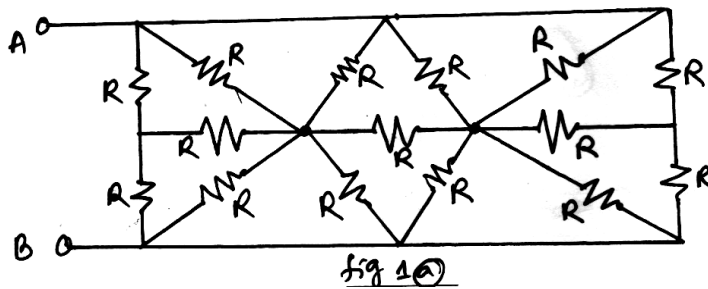1 a. Find an equivalent resistance at terminals AB in Fig. 1(a).




9 L3 CO2 PO2

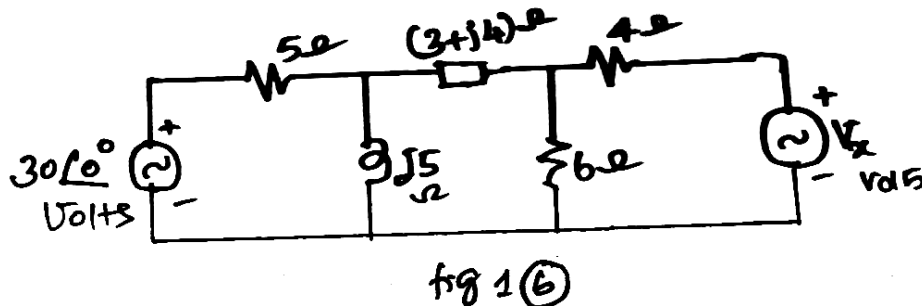b. Find the source voltage V_x in the Fig. 1(b), using KVL method, if current through the impedance $(3+j4) \Omega$ is zero.



9 L3 CO2 PO2

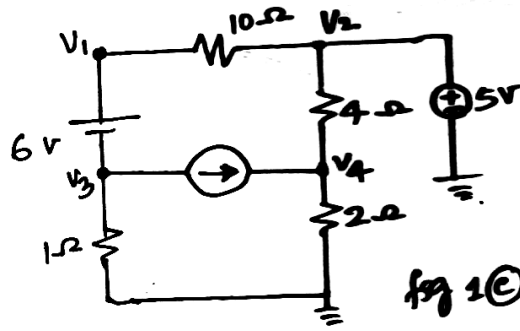c. Determine all the nodal voltages in the Fig.1(c) shown, using KCL.



9 L4 CO2 PO2

UNIT - II


18

2 a. Show that a two branch parallel circuit is resonant at all frequencies, if

$$R_L = R_C = \sqrt{\frac{L}{C}} \Omega.$$

9 L2 CO2 PO1

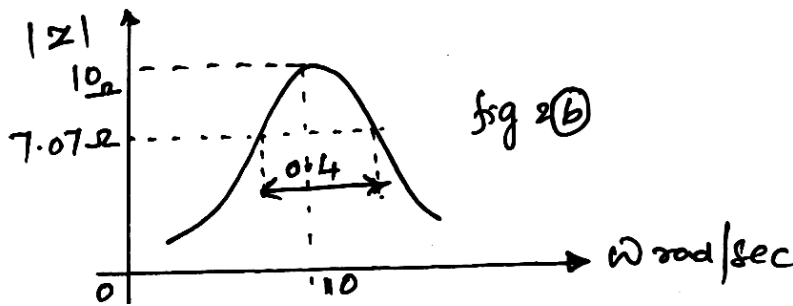
b. Determine the RLC parallel circuit parameters whose response curve is as shown in Fig. 2(b). What are the new values of ω_r and bandwidth if C is increased four times?



9 L2 CO2 PO2

c. The network shown in the Fig. 2(c) is in steady state with the switch k closed. At $t = 0$, the switch is closed. Determine the voltage across the switch

V_X and $\frac{dV_k}{dt}$ at $t = 0^+$

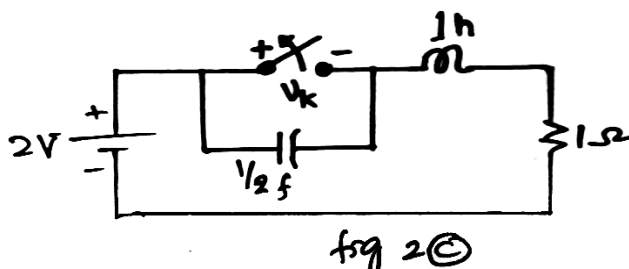

9 L3 CO2 PO2

UNIT - III

18

3 a. Deduce the Laplace transform of the following:

i) $\cosh(\omega t)$

9 L2 CO3 PO2


ii) $\sin \omega t$

iii) $e^{-at} \cdot \cos \omega t$

b. Find the inverse Laplace transform of $f(s) = \frac{1}{s(s^2 - 2s + s)}$.

9 L2 CO3 PO2

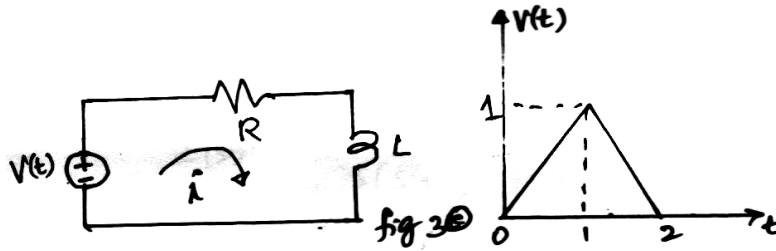- c. A triangular wave is applied input to series RL circuit with $R = 2 \Omega$, $L = 2 \text{ H}$ as shown in Fig. 3(c). Calculate the current $i(+)$ through the circuit.




9 L2 CO3 PO2

UNIT - IV


18

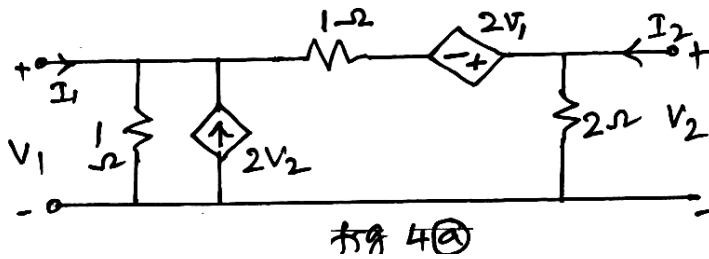- 4 a. Determine ABCD parameters for the network shown in Fig. 4(a).



9 L4 CO4 PO2

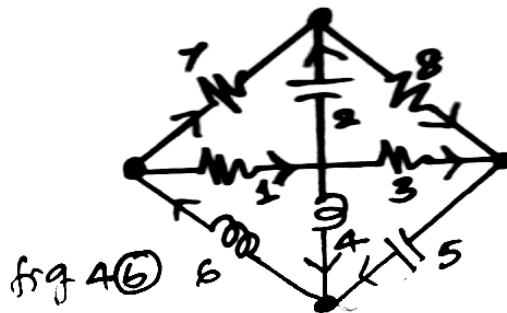- b. In the network shown in Fig. 4(b) consider the branches 1, 2, 3, 4 forming a tree. Determine the branch current in terms of the loop current.



9 L4 CO4 PO2

- c. Define Z parameters and Y parameters of the two port network. Derive Y parameters in terms of Z parameters. What is reciprocal and symmetry condition of a passive network?

9 L3 CO4 PO3

UNIT - V

18

- 5 a. Test whether,

9

$$F(S) = \frac{2S^4 + 7S^3 + 11S^2 + 12S + 4}{S^4 + 5S^3 + 9S^2 + 11S + 6}$$

is positive real functions?

L2 CO5 PO3

- b. Realize / Synthesize Causer second form of the LC driving point impedance

9

$$\text{function } Z(S) = \frac{(S^2 + 1)(S^2 + 16)}{S(S^2 + 4)}$$

L2 CO5 PO3

- c. Realize the foster first form of the RC impedance function

9

$$Z(S) = \frac{(S + 1)(S + 3)(S + 5)}{S(S + 2)(S + 4)(S + 6)}$$

L2 CO5 PO3