



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
Third Semester, B.E. - Electrical and Electronics Engineering
Semester End Examination; March - 2021
Electric Circuit Analysis

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1: To solve problems on electrical network using different techniques and theorems, resonance concepts.

CO2: To obtain graphical solution to electrical networks using Network Topology.

CO3: Analyze the network under transient condition due to switching.

CO4: Analyze and obtain the time domain response of R, L, C circuits for all types of excitations using Laplace transforms.


CO5: Represent the two port networks by Z,Y, ABCD and Parameters and Assessment of stability of network from network function.

Note: I) PART - A is compulsory. Two marks for each question.

II) PART - B: Answer any Two sub questions (from a, b, c) for Maximum of 18 marks from each unit.

Q. No.	Questions	Marks	BLs	COs	POs
	I: PART - A	10			

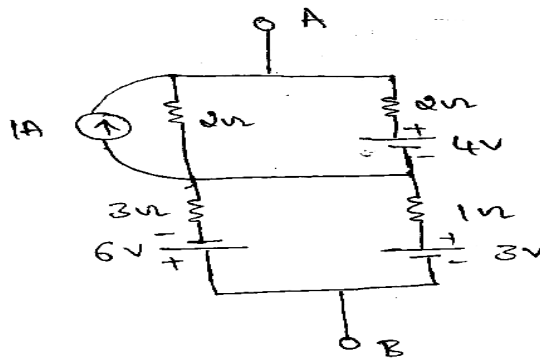1 a. Replace the given network with a single voltage source and resistor between terminals A and B.



2


b. What are the conditions for series resonance?

2

c. Find inverse Laplace transform of the function $F(s) = \frac{s^2 - 3s + 4}{s^3}$.

2

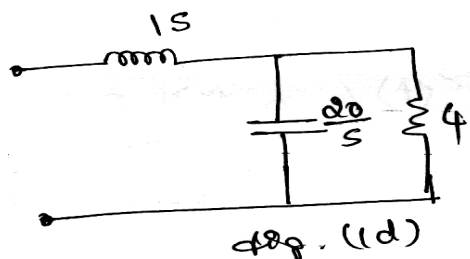d. Find driving point admittance function of the following network shown in Fig. (1d).



2

e. Define two port networks and give the classification of two port network parameters.

2


II: PART - B

90

UNIT - I


18

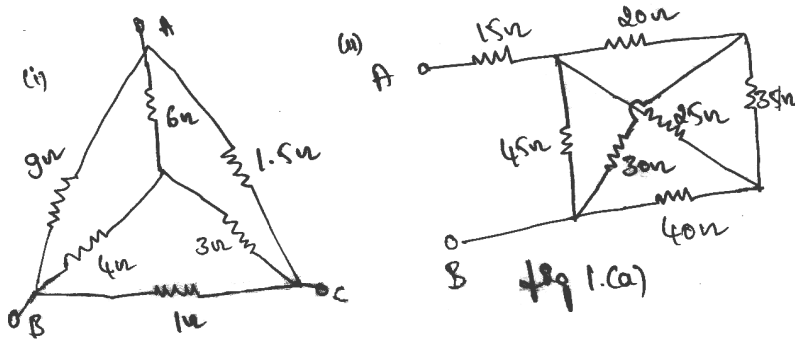1 a. Find an equivalent resistance between A and B of the networks shown in Fig. 1(a).




9

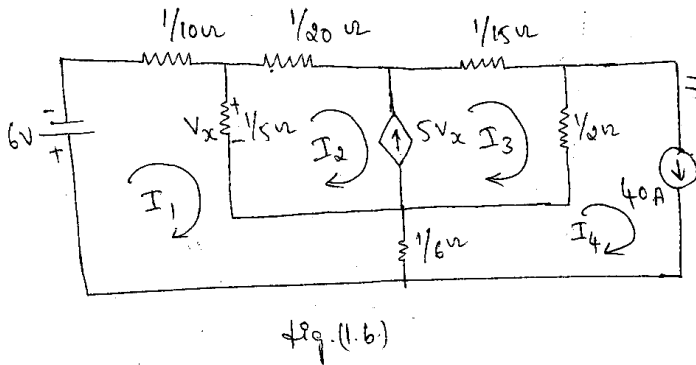b. Find Currents I_1, I_2, I_3 and I_4 for the network shown in Fig. (1.b).



9

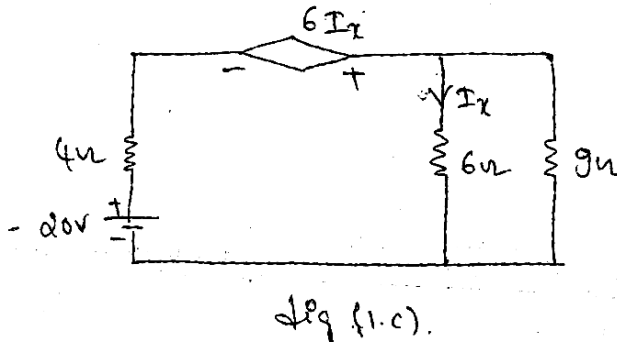c. Find the current through 9 Ω resistor using Thevenin's theorem for the circuit shown in Fig. (1.c).




9

UNIT - II

18

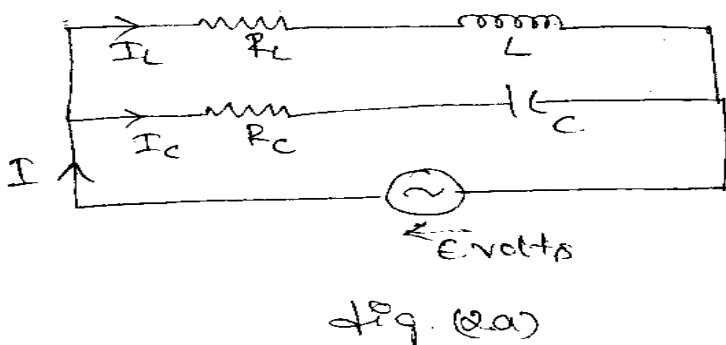2 a. Derive an expression for resonant frequency and current at resonance for the network shown in Fig. (2.a).



9

b. A series RLC circuit has a resistance of 10Ω , an inductance of 0.3 H and a capacitance of $100 \mu\text{F}$. The applied voltage is 230 V . Find;

- i) The resonant frequency
- ii) The quality factor
- iii) Lower and upper cut off frequencies
- iv) Bandwidth
- v) Current at resonance
- vi) Currents at f_1 and f_2
- vii) Voltage across inductance at resonance

c. A series RL circuit consists of a resistance of 5Ω and inductance of 0.02 H is connected across the voltage $V = (100 + 50 \sin 500t + 25 \sin 1500t) \text{ V}$. Find;

- i) Current
- ii) Average power
- iii) Power factor


Also write the expression for the current in the circuit.

UNIT - III

18


3 a. For the network shown in Fig. (3.a) the switch is changed from position (1) to (2) at $t = 0$ steady state having reached before switching. Find the value

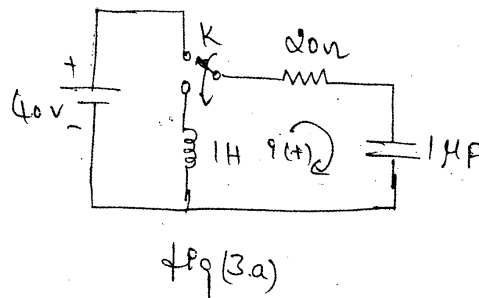of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$.




9

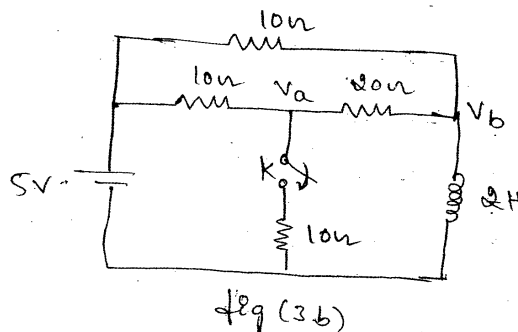b. In the network shown in Fig. (3.b) a steady state is reached with the switch 'K' open. At $t = 0$, the switch is closed. For the elemental values given. Determine the value of $V_a(0^-)$, $V_a(0^+)$ and $V_b(0^+)$.



9

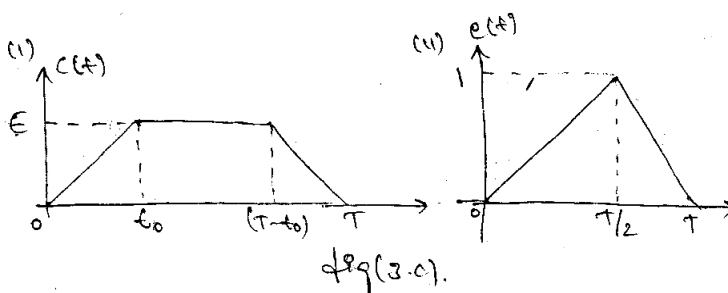c. Write the equation for the waveforms shown in Fig. (3.c) and find its Laplace transform.



9

UNIT - IV

18

4 a. A balanced star connected load of 150 kW having an impedance of $6.351\angle 38.06^\circ \Omega$ is connected to a 3 ϕ , 4 wire, 1100 V RYB system. Find the line currents, circuit constants of the load per phase and also draw the vector diagram.

9

b. Currents I_1 and I_2 entering at port 1 and port 2 respectively of a two port networks are given by the following equations:

9

$$I_1 = 0.5 V_1 - 0.2 V_2 \quad I_2 = -0.2 V_1 + V_2$$

Find Y, Z and $ABCD$ parameters for the network.

c. Obtain the following:

i) z -parameter in terms of y -parameters


9

ii) h -parameters in terms of z -parameters

UNIT - V


18

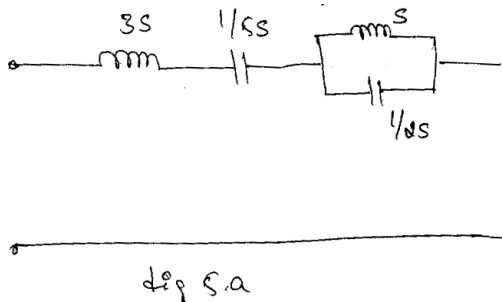5 a. Find the driving point admittance for the network shown in Fig. (5.a).



9

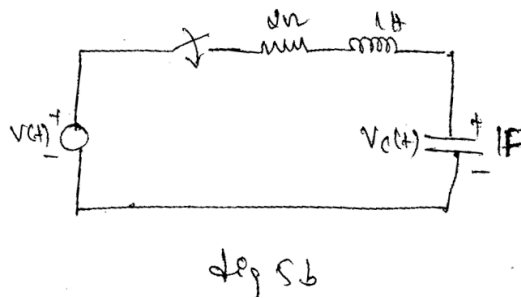b. Find the impulse response of the voltage across the capacitor in the network shown in fig. 5b, also determine response $V_c(t)$ for step input.




9

c. Determine the expression for $V_L(t)$ in the network shown in Fig. (5.c) when,

i) $V_s(t) = \delta(t)$

ii) $V_s(t) = e^{-t} u(t)$

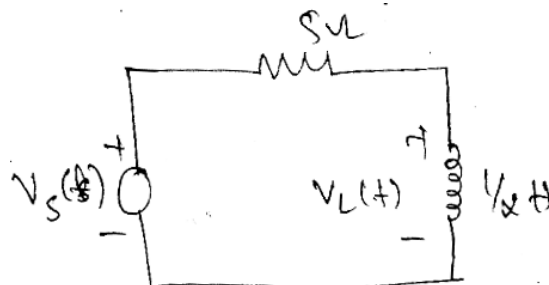

9