



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

First Semester, B.E. - Semester End Examination; Dec. - 2019

Basic Electronics


(Common to all Branches)

Time: 3 hrs

Max. Marks: 100

Note: i) PART - A is compulsory. **Two** marks for each question.

ii) PART - B: Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

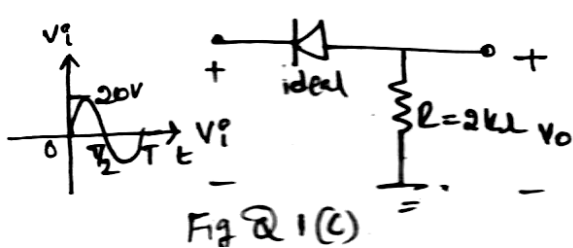Q. No.	Questions	Marks
I : PART - A		10
I a.	What is DC load line? Write the diode circuit equation.	2
b.	Write the structure of an n-channel depletion type MOSFET.	2
c.	List the ideal characteristics of Op-Amp.	2
d.	Write the 1's and 2's compliment of $(10110)_2$.	2
e.	Define amplitude modulation and draw modulated signal.	2
II : PART - B		90
UNIT - I		18
1 a.	Write a neat circuit diagram and waveform, explain the working of center tapped full wave rectifier and write the expression for average DC output voltage V_{dc} .	9
b.	Explain the DC load line analysis for series diode configuration with neat circuit diagram and characteristic.	9
c.	Solve the following :	
	i) Sketch the output V_o and determine the average DC level of the output for the network of Fig.Q.1(c).	9
 <p style="text-align: center;">Fig Q 1(c)</p>		
	ii) Repeat part (i) if the ideal diode is replaced by a silicon diode	
	iii) Repeat part (i) and (i) if V_m is increased to 200 V and compare solutions using equations	
UNIT - II		18
2 a.	With neat diagram, explain the construction and operation of a CMOS inverter.	9
b.	Explain the construction and characteristics of an n-channel enhancement type MOSFET with a necessary diagram.	9
c.	Write the MOSFET amplifier circuit with voltage divider bias. Obtain the equation for Z_i , Z_o and A_v using AC equivalent model. Use n-channel D-type MOSFET.	9

UNIT - III**18**

- 3 a. Explain the following controlled source:
- i) Voltage Controlled Voltage Source 9
 - ii) Voltage Controlled Current source 9
 - iii) Current Controlled Current source
- b. What are active filters? Explain the types in detail with necessary diagram. 9
- c. Explain how Op-Amp can be used as?
- i) Integrator 9
 - ii) Inverting summing amplifier
 - iii) Voltage follower

UNIT - IV**18**

- 4 a. Convert the following:
- i) $(725.25)_{10} = (?)_2 = (?)_{16}$ 9
 - ii) $(111100111110001)_2 = (?)_{10} = (?)_{16}$
 - iii) Binary subtraction using 2's complement of $(22-17)_{10}$
- b. Simplify and realize the following using basic gates only:
- i) $Y = AC + ABC + \overline{ABC} + AB + D$ 9
 - ii) $Y = (B + CA)(C + \overline{AB})$
- c. Realize the following:
- i) OR using NAND only 9
 - ii) AND using NOR only
 - iii) XOR using NAND only

UNIT - V**18**

- 5 a. Define AM. Draw an AM signal and its spectrum. Derive an expression for total power in an AM signal. 9
- b. Explain super hetero dyne receiver used in radio receivers with neat diagram. 9
- c. Write a short note:
- i) Resistive transducer 9
 - ii) Thermo electrical transducer

* * *