

U.S.N 

--	--	--	--	--	--	--	--	--	--

**P.E.S. College of Engineering, Mandya - 571 401***(An Autonomous Institution affiliated to VTU, Belagavi)***Third Semester, B.E. - Electronics and Communication Engineering****Semester End Examination; Dec. - 2019****Digital Electronic Circuits**

Time: 3 hrs

Max. Marks: 100

**Note:** i) **PART - A** is compulsory. **Two** marks for each question.ii) **PART - B:** Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

Q. No.	Questions	Marks
<b>I : PART - A</b>		<b>10</b>
I a.	Define canonical minterm and canonical maxterm.	2
b.	What are the differences between synchronous and asynchronous counters?	2
c.	Draw the schematic of full adder using two half adders.	2
d.	What is race around condition in JK flip-flop? When does it occur?	2
e.	Compare Moore and Mealy models.	2
<b>II : PART - B</b>		<b>90</b>
<b>UNIT - I</b>		<b>18</b>
1 a.	Simplify the following Boolean expressions using k-map:	
i)	$f(ABCD) = \overline{A}BC + AD + B\overline{D} + C\overline{D} + A\overline{C}$	9
ii)	$F(wxyz) = (w+x+y) \cdot (\overline{x+z}) \cdot (\overline{w+y}) \cdot (x+y)$	
b.	Find the minimal sum of the Boolean expression using Quine-McCluskey method, $f = \sum m(1, 3, 6, 8, 9, 10, 12, 14) + \sum d(7, 13)$	9
c.	Simplify the following expressions using VEM technique:	
i)	$f(ABCD) = \sum m(2, 3, 5, 6, 8, 11, 12, 13)$	9
ii)	$Y = \overline{A}BCD + \overline{A}BCDE + \overline{A}BCDE + \overline{A}BCD + ABC\overline{D} + ABC\overline{D}F + \overline{A}BC\overline{D}F + ABCDE$	
<b>UNIT - II</b>		<b>18</b>
2 a.	i) Implement Full subtractor using a suitable decoder.	9
	ii) Design a 2 bit comparator and implement using basic gates.	
b.	Implement $f = ad + \overline{bc} + bd$ using (i) 16:1 MUX (ii) 8:1 MUX (iii) 4:1 MUX	9
c.	Write a short note Read Only Memory (ROM) and Programmable Logic Array (PLA).	9

**UNIT - III**

**18**

- 3 a. Derive the characteristic equations of SR Flip flop and JK Flip flop. 9
- b. Explain the operation of Master-Slave JK flip flop using the logic diagram, truth table and clock diagram. 9
- c. Convert; (i) SR Flip flop to JK Flip flop (ii) JK flip flop to D flip flop 9

**UNIT - IV**

**18**

- 4 a. Explain with suitable logic diagram and truth table the operation of the following shift registers: 9
  - (i) Serial-in-Serial-out
  - (ii) Serial-in-Parallel-out
  - (iii) Parallel-in-Serial-out
  - (iv) Parallel-in-Parallel out
- b. Design a counter using JK flip flop to count the following sequence 9  
 $0 \rightarrow 1 \rightarrow 3 \rightarrow 7 \rightarrow 6 \rightarrow 4 \rightarrow 0$
- c. Design an arithmetic circuit with two select lines  $S_1$  and  $S_0$  that generates the following arithmetic operations. Draw the logic diagram. 9


$S_1$	$S_0$	$C_{in} = 0$	$C_{in} = 1$
0	0	$F = A$	$F = A + 1$
0	1	$F = A + B$	$F = A + B + 1$
1	0	$F = A + \bar{B}$	$F = A + \bar{B} + 1$
1	1	$F = A - 1$	$F = A$

9

**UNIT - V**

 **18**

- 5 a. For the logic diagram given below:
  - i) Write the excitation table and derive the output equations
  - ii) Write the next state equations
  - iii) Construct a transition table
  - iv) Draw the state diagram



9

- b. Design a Mealy type sequence detector to detect a serial input 101 (use D F/F). 9
- c. Differentiate Mealy state machine and Moore State machine. 9