



**P.E.S. College of Engineering, Mandya - 571 401**  
 (An Autonomous Institution affiliated to VTU, Belagavi)  
**Third Semester, B.E. - Electronics and Communication Engineering**  
**Semester End Examination; Dec. - 2019**  
**Network Analysis and Synthesis**


Time: 3 hrs

Max. Marks: 100



**Note: i) PART - A** is compulsory. **Two** marks for each question.

**ii) PART - B:** Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

Q. No.	Questions	Marks
<b>I : PART - A</b>		
I a.	State Thevenin theorem.	2
b.	Define bandwidth and selectivity of a series RLC circuit.	2
c.	Find the Laplace transform of damped hyperbolic sine function $e^{-at} \sin(\omega t)$ .	2
d.	Define the following: i) link            ii) sub-graph	2
e.	Determine whether the polynomial $P(s) = s^3 + 3s^2 + 2s + 1$ is Hurwitz or not.	2
<b>II : PART - B</b>		
<b>UNIT - I</b>		
1 a.	Find the nodal voltage in the circuit.	18

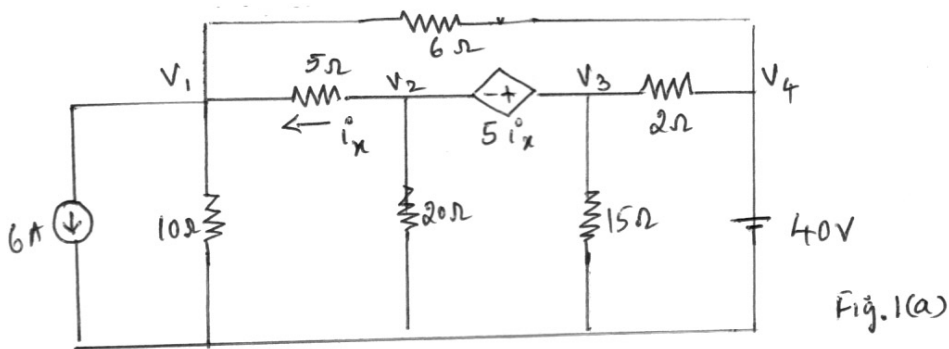

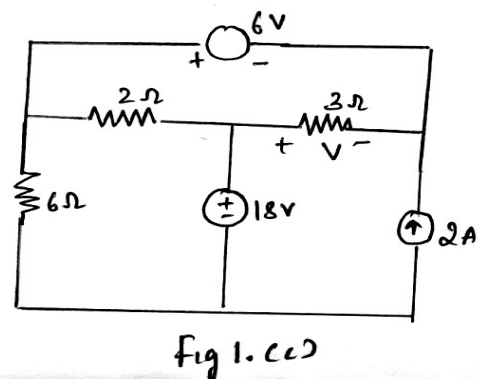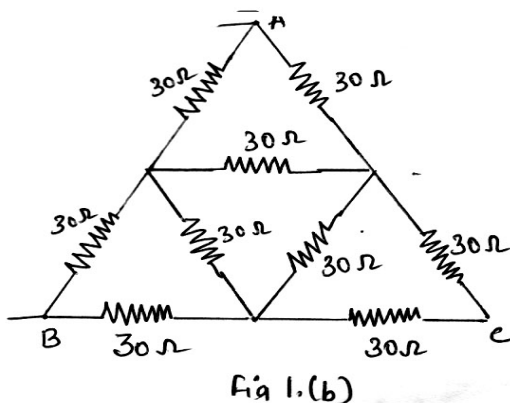b. Find equivalent resistance at terminal AB in Fig.1(b)




- c. Find the voltage 'V' across 3 Ω resistor using super position theorem for the circuit given in Fig.1(c). 9

**UNIT - II**

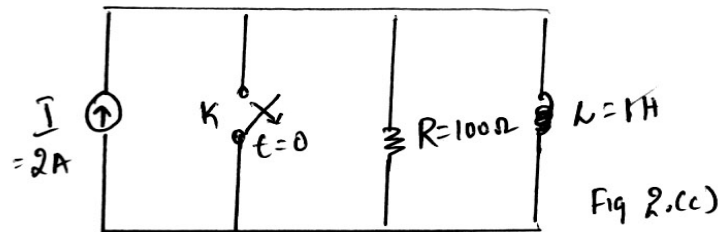**18**

- 2 a. What is resonance? Show that resonant frequency of series resonance circuit is equal to geometric mean of two half power frequencies. 9
- b. A parallel resonant circuit has a coil of 150 μH with Q factor of 100 and is resonated at 1 M Hz;
- i) Specify the required value of capacitance
  - ii) What is resistance of coil? 9
  - iii) What is resistance of circuit at parallel resonance?
  - iv) What is absolute band width of resonant circuit?
- c. Determine  $v, \frac{dv}{dt}, \frac{d^2v}{dt^2}$  at  $t = 0^+$  when the switch  $k$  is opened at  $t = 0$  for the Fig. 2(c).



**UNIT - III**

**18**

- 3 a. Use initial and final value theorem to find  $f(0)$  and  $f(\infty)$  for the following :
- i)  $F(s) = \frac{s^3 + 7s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)}$
  - ii)  $F(s) = \frac{e^{2s}}{s^2 + 5}$  9
  - iii)  $F(s) = \frac{s(s+4)(s+8)}{(s+1)(s+6)}$
- b. Find the inverse Laplace transform of  $f(s) = \frac{2s+4}{(s^2+4s+13)}$ . 9
- c. In the series RL circuit shown in Fig.3(c) the source voltage is  $V(t) = 50 \sin 250t$  V. Determine the resulting current, if the switch is closed at  $t = 0$ . 9

**UNIT - IV**

**18**





- 4 a. Define Z parameters for the network shown in Fig. 4(a). 9
- b. Determine the transmission parameters for the network shown in the Fig.4 (b). 9
- c. In the network shown in Fig.4(c) consider branches 1, 3, 4 forming a tree. Write a tie set schedule and hence write equilibrium equation on loop current basis and find values of loop currents consider that the branch number indicates value of resistance in that branch. 9

UNIT - V

5 a. Test whether  $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$  is positive real function. 9

b. Realize foster form-II for the following LC impedance function  $Z(s) = \frac{(s^2 + 1)(s^3 + 3)}{s(s^2 + 2)(s^2 + 4)}$ . 9

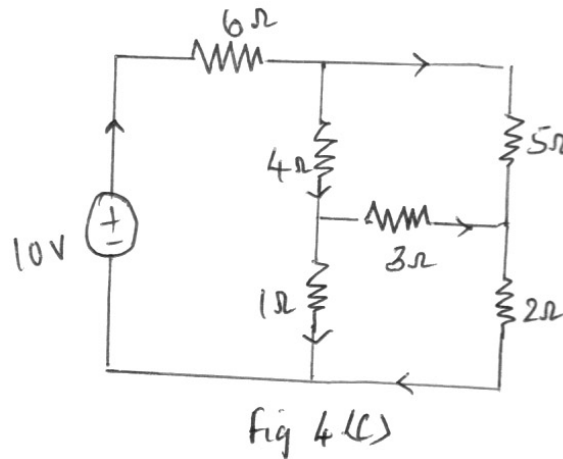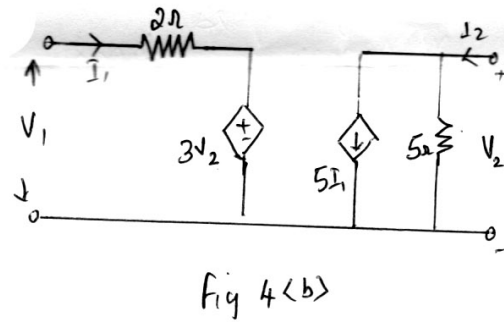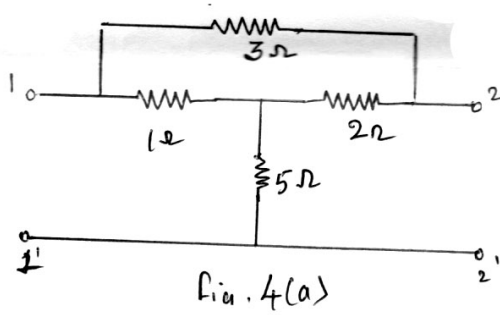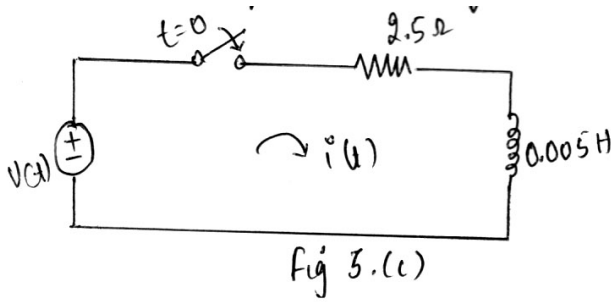c. Realize caver foster-I forms for the following RC impedance function  $Z(s) = \frac{s + 4}{(s + 2)(s + 6)}$ .



\*\*\*