



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec. - 2019

Electrical Circuit Analysis

Time: 3 hrs

Max. Marks: 100

Note: i) **PART - A** is compulsory. **Two** marks for each question.

ii) **PART - B:** Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

Q. No.	Questions	Marks
I : PART - A		10
I a.	Explain the concept of super Mesh in the analysis of network using mesh analysis.	2
b.	List out the conditions to be satisfied by a periodic function $f(t)$ for the existence of its Fourier series.	2
c.	What are initial conditions in a network? Explain importance of their determination in a network.	2
d.	Find whether following network function represent driving point immittance function? If not, List the errors.	2
	$F_1(S) = \frac{4S^4 + S^2 - 3S + 1}{S^3 + 2S^2 + 2S + 40}$	
e.	What is meant by unit impulse function and find its Laplace Transform?	2

II : PART - B	90
----------------------	-----------

UNIT - I	18
-----------------	-----------

1 a. In the network shown in Fig. 1(a), use nodal technique to determine i_x .

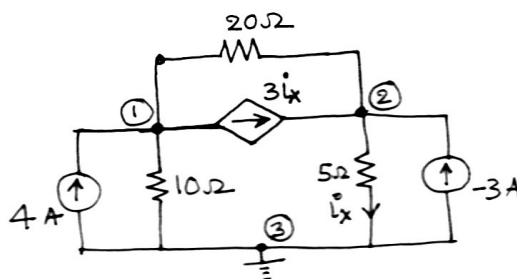


Fig. 1(a)

b. In the network shown in Fig. 1(b), use mesh equations to find the mesh currents i_1 , i_2 and i_3 as assigned.

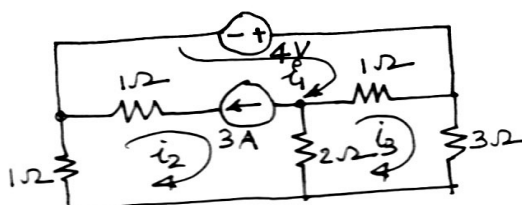


Fig. 1(c).

- c. Find the Thevenin's equipment network across the terminals A and B of the network shown in Fig.1(c).


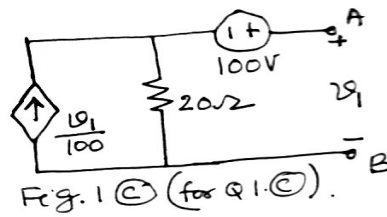


Fig .1(c).

UNIT - II

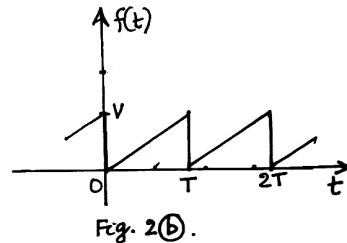
- 2 a. A series RLC circuit has $Q_0 = 5.1$ at its resonant frequency of 100 kHz. Assuming the power dissipation of the circuit is 100 W when drawing a current of 0.8 A, find;
- i) RLC ii) Bandwidth Δf iii) Half power frequencies f_1 and f_2
- b. Find the Fourier series for the waveform shown in Fig .2(b) Assume $V = 10V$, $T = 1s$. (Trigonometric Fourier series)



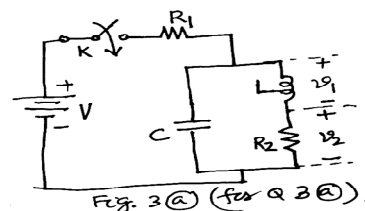
- c. A voltage given by $V = 50 + 50\sin(5000t) + 30\sin(10000t) + 20\sin(20000t)$ is applied to a circuit consisting of two elements in series. The current is;
- $$I = 11.2 \sin(5000t + 63.4^\circ) + 10.6 \sin(10000t + 45^\circ) + 8.97\sin(20000t + 26.6^\circ).$$
- Find; i) Average power ii) Constants as parameter of the circuit.

UNIT - III


- 3 a. Fig. 3(a) shows a network with zero capacitor voltage and zero inductor current, when the switch K is open. At $t = 0$ the switch K is closed. Solve for;
- i) V_1 and V_2 at $t = 0^+$ ii) $\frac{dV_1}{dt}$ and $\frac{dV_2}{dt}$ at $t = 0^+$ iii) V_1 and V_2 at $t = \infty$.



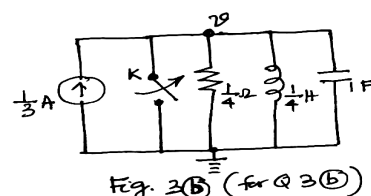- b. Fig. 3(b) shows a RLC parallel circuit excited by a dc current source. At $t = 0$, the switch K is opened. Find $V(t)$.



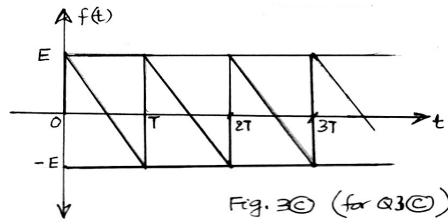c. Find the Laplace transform of the periodic saw tooth wave shown in Fig 3(c).



9

UNIT - IV

18

4 a. The h-parameter of a certain two port network are $h_{11} = 1 \Omega$, $h_{12} = 2$, $h_{21} = -2$, $h_{22} = 1 \Omega$ Find;
 i) Z-parameters ii) Y-parameters iii) ABCD parameters
 Find whether the network is reciprocal, symmetrical.


9

b. A star connected 3- ϕ load has a resistance of 8Ω and a capacitive reactance of 10Ω in each phase. It is fed from a 400 V, 3- ϕ balanced supply.

9

i) Find the line current, total VA, active and reactive power ii) Draw Phasor diagram

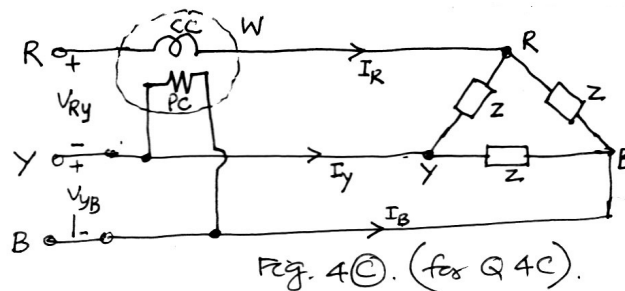c. A balanced delta connected/load shown in Fig.4(c) takes a line current of 15 A, when connected to a balanced 3- ϕ , 400 V system. A wattmeter with its current coil in one line and its pressure coil between the two remaining lines reads 2000 W. Describe the load impedance.




9

UNIT - V

18

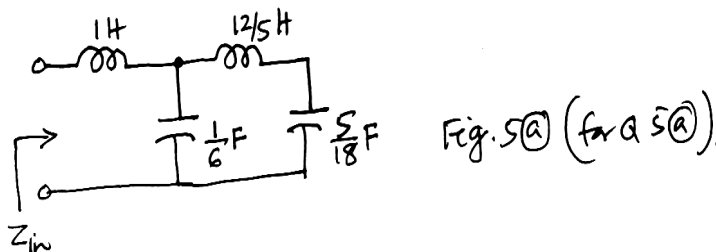5 a. For the network shown in Fig. 5(a), find the driving point input impedance. Plot the Pole-Zero patterns of network shown.



9


b. Fig. 5(b) shows an RC circuit consisting of two capacitors and one resistance.

$C_1 = 10 \mu F$, $C_2 = 40 \mu F$ and $R = 0.5 M\Omega$. There is initial charge on C_1 such that voltage across its terminals is 200 V. At $t = 0$ the switch 'K' is closed.

9

i) Find time domain voltage expressions for voltages across the two capacitors

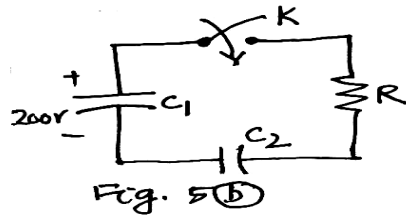
ii) Find the steady state voltages across these capacitors. Use Laplace transformation method.



c. A series circuit has a resistance of 4Ω and an inductance of 0.1 H as shown in Fig. 5(c). The switch K is closed at $t = 0$ by exciting the circuit by the voltage sources when,

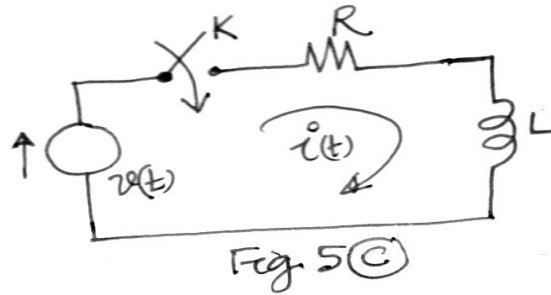- i) Unit impulse V_g of $\delta(t-3)$
- ii) A unit ramp voltage $r(t-3)$

Find the current $i(t)$ for each source separately i.e. Taking one at a time.



9
