



**P.E.S. College of Engineering, Mandya - 571 401**  
 (An Autonomous Institution affiliated to VTU, Belagavi)  
**Third Semester, B.E. - Information Science and Engineering**  
**Semester End Examination; Dec. - 2019**  
**Digital Design**

Time: 3 hrs

Max. Marks: 100

**Note:** I) **PART - A** is compulsory. **Two** marks for each question.

II) **PART - B:** Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

Q. No.	Questions	Marks
	<b>I : PART - A</b>	<b>10</b>

I a. What is the Boolean function obtained for the following truth table:

<i>x</i>	<i>y</i>	<i>f(x, y)</i>
0	0	0
0	1	0
1	0	1
1	1	1

2

b. Obtain the minimal form from the K-map


	<i>bc</i>			
a	1	X	X	1
			1	X

2

c. Give the excitation table of JK flip flop.

2

 d. What does the following gate gives the output?



2

e. What is the number of flip flops required to design mod-200 counter

2

<b>II : PART - B</b>		<b>90</b>
<b>UNIT - I</b>		<b>18</b>

1 a. Express  $-19,750$  is 2's complement representation. Then show how this number is stored at address 2000. Use hexadecimal notation to compression the data.

9

b. Design a combinational circuit whose output is 1 for the binary number  $> 5$  and  $< 10$  and numbers from 10 - 15 are don't care condition.

9

c. Define universal gates. Implement the following function:

i) Nand gates only

ii) Nor gates only

iii) Nor gates only

9

$$g = x'y + xy + xy'$$

**UNIT - II**

**18**

2 a. Simplify the given SOP expression using Quine McCluskey method:

9

$$F(a, b, c, d) = \sum m(2, 3, 10, 11, 12, 13, 14, 15) + d(0, 1)$$

b. Realize the following expression using decoder:

9

i)  $f = xy + x'y + xy'$       ii)  $f = xyz + x'z + xy$       iii)  $f = x'z + x'y + z'$

c. Implement the following using PLA

$$f(A, B, C) = \sum m(0, 2, 4, 5, 6)$$

9

$$f(A, B, C) = \sum m(0, 1, 3, 5)$$

**UNIT - III**

**18**

3 a. Discuss half subtractor and Full subtractor with a neat logic circuit.

9

b. Discuss the operation of JK flip flop with truth table and design the JK flip flop circuit using only Nand gates.

9

c. Convert the following:

9

i) RS flip flop to JK flip flop      ii) JK flip flop to T flip flop

**UNIT - IV**

**18**

4 a. Explain the operation of 4-bit serial in serial out shift register with neat circuit diagram for 4-bit data 1011.

9

b. Design a mod-6 counter using decade CD user and also explain the circuit diagram and truth table of decade counter.

9

c. Determine the number of possible states in a counter composed of the following number of flip flops: i) 8      ii) 7      iii) 9

9


**UNIT - V**

**18**

5 a. Differentiate between Moore Model and Mealy model with appropriate state transition diagrams.

9

 b. Reduce state transition diagram using row elimination method and Implication Table method.



9

c. How can essential Hazard to be prevented in asynchronous sequential circuits.

9

\* \* \*