



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Eighth Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; July - 2021


Data Acquisition and Instrumentation

Time: 3 hrs

Max. Marks: 100

Note: Answer any **FIVE** full questions.

- 1 a. Draw the schematic block diagram of a generalized data acquisition system and explain. 10
- b. Discuss the objectives of DAS and computer based DAS. 10
- 2 a. For a 5 bit resistive divider, determine the following , (Assuming 0 = 0 and 1 = +10 V)
 - i) The weights assigned to the LSB
 - ii) The weights assigned to the 2nd and 3rd LSB 10
 - iii) The change in output voltage due to the change in the LSB, 2nd LSB and 3rd LSB
 - iv) The output voltage for a digital input of 11011 and 10110
- b. With a neat diagram, explain the operation of a R-2R ladder type digital to analog converter. 10
- 3 a. Define strain gauges and classify different types of strain gauges. 10
- b. What are the factors required while selecting a transducers? 6
- c. What is the thermistor? Mention its advantages. 4
- 4 a. Describe the operation of piezo-electric transducers. 6
- b. Explain the operation of photo-transistor with an application. 4
- c. Explain the construction, principle, and operation of Linear Variable Differential Transducers (LVDT). 10
- 5 a. Explain the static characteristics of an instrument. 10
- b. The expected value of the current through a resistor is 20 mA. However the measurement yields a current value of 18 mA. Calculate;
 - i) Absolute error
 - ii) %age error
 - iii) Relative accuracy
 - iv) %age accuracy
- 6 a. Calculate the value of multiplier resistance for the multiple range dc voltmeter circuit shown in the figure. 10

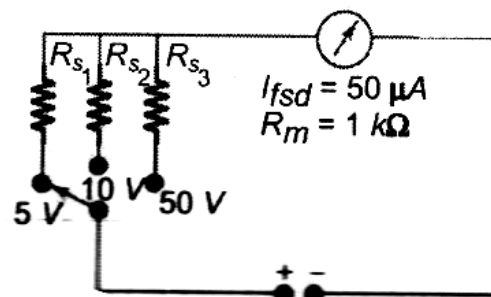

- b. With a neat diagram, explain the operation of a True RMS voltmeter. 10

- 7 a. With necessary waveforms and block diagram, explain the working of a ramp type DVM. 10
b. With necessary waveforms and block diagram, explain the working of a successive approximation type DVM. 10
- 8 a. Explain the working of a digital multimeter with neat block diagram. 10
b. Explain the working of a digital frequency meter with neat block diagram. 10
- 9 a. List any five ideal Op-amp electrical characteristics. 5
b. Draw an Op-amp inverting amplifier with feedback and derive its closed loop voltage gain. 5
c. Explain the working of an electronic-aided measurement with a neat block diagram. 10
- 10 a. The chart speed of a recording instrument is 40 mm/s. One cycle of the signal is recorded over 5 mm. Determine the frequency of the signal. 5
b. How is the speed of the paper through the recorder determined? Why is paper speed an important consideration? Give reasons. 5
c. Explain the working of a strip chart recorder with a neat block diagram. 10

* * * *