

U.S.N



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Sixth Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; July / Aug. - 2022

Analog CMOS VLSI Design

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1 - Apply the knowledge of physics circuit elements and circuit analysis to understand the MOS devices and analog CMOS.

CO2 - Analyse different analog CMOS VLSI circuits amplifiers, Op-amps, Oscillators.

CO3 - The Design the analog CMOS circuits for the given Specifications.

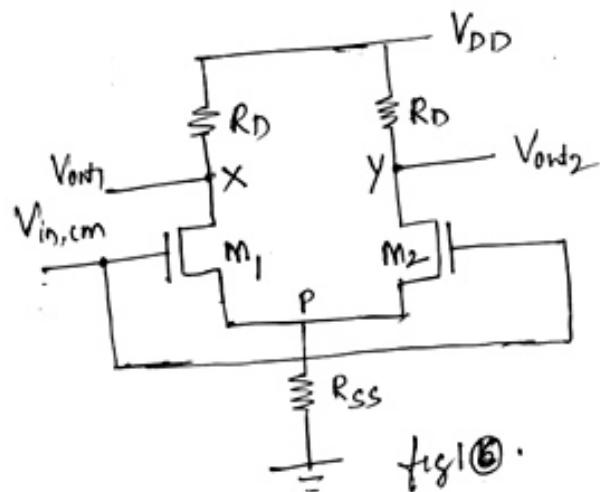
CO4 - The Develop analog CMOS circuits for Different applications.

CO5 - To Simulate the analog CMOS circuits using modern tools.

Note:I)PART - A is compulsory. Two marks for each question.

II)PART - B: Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

Q. No.	Questions	Marks	BLs	COs	POs
	I : PART - A	10			
I a.	Give the advantages of cascade stage over simple common source amplifier.	2	L1	CO1	PO1
b.	Sketch the small signal differential gain of a differential pair as a function of the input CM level.	2	L1	CO2	PO2
c.	Calculate the pole associated with node x shown in fig. a				
		2	L2	CO2	PO2
d.	List any two drawbacks of the telescopic cascade op amps.	2	L1	CO1	PO1
e.	Define VCO.	2	L1	CO1	PO1
	II : PART - B	90			
	UNIT - I	18			
I a.	Derive an expression for voltage gain and output resistance of common source stage with source degeneration $\lambda \neq 0$ and $\gamma \neq 0$.	9	L2	CO4	PO3
b.	For the source follower obtain the expression for small single voltage gain and output resistance taking $\lambda = 0$.	9	L2	CO2	PO2
c.	For the circuit shown below Fig.1c find ACM-DM (common mode to differential mode conversion). M1 and M2 are not identical, $R_{D1} = R_{D2} = R_D$.	9	L1	CO1	PO1

**UNIT - II****18**

- With neat circuit diagram, explain Gilbert cell.
- Explain the basic current mirror with relevant equation? Explain how channel length is eliminated?
- With neat circuit diagram, explain the operation of Cascode current mirror.

9 L2 CO2 PO2


9 L2 CO2 PO2

9 L2 CO2 PO2

UNIT - III**18**

- Explain miller effect. calculate the input capacitance of the circuit


Fig. 3 (a) by using miller's theorem.

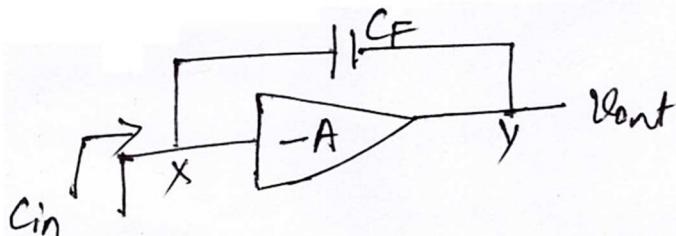

9 L2 CO2 PO2

Fig. 3 (a)

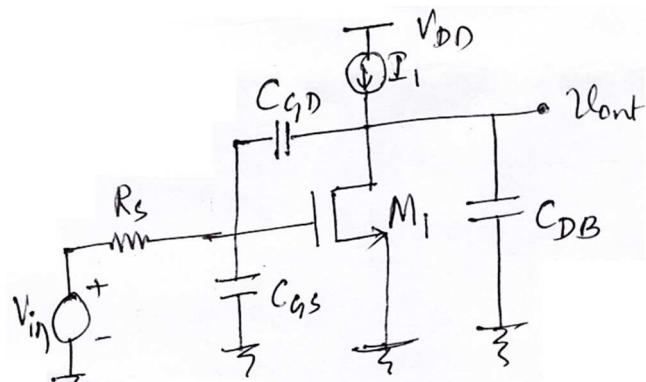- For the circuit shown in Fig 3. (b), calculate the transfer function ($\lambda = 0$) and explain why miller effect vanishes on C_{DB} increases?



9 L3 CO4 PO3

Fig 3 (b)

- With neat diagram derive the input And output impedance and transfer function of a source followers.

9 L5 CO4 PO3

UNIT - IV

18

- 4 a. Explain briefly the following performance parameter of a OP-amp:


- i) Gain
- ii) Small single B.W
- iii) Output swing
- iv) Noise and offset

9 L2 CO2 PO2

- b. Explain the operation and advantages of two stage OP-amp with a neat circuit diagram.

9 L2 CO2 PO2

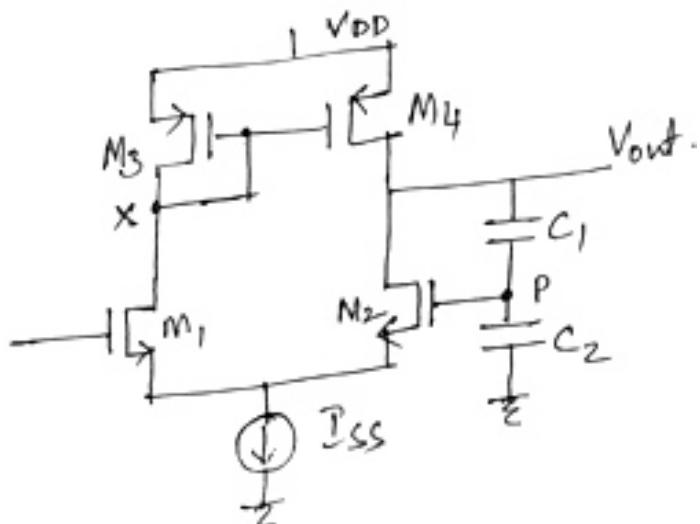- c. Define PSRR. Calculate the low frequency PSRR of the feedback circuit shown in Fig. 4 (c).



9 L2 CO2 PO2

Fig. 4 (c).

UNIT - V

18

- 5 a. Write a short note on;

- i) Thermal Noise
- ii) Flicker Noise

9 L1 CO2 PO2

- b. With a neat circuit diagram, design and explain a 3-stage ring-oscillator.

9 L2 CO3 PO4

- c. Explain the important performance parameter of VCOS.

9 L2 CO2 PO2

* * * *