



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
Second Semester, B.E. - Semester End Examination; July/Aug. - 2022
Basic Electrical Engineering
 (Common to all Branches)

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1: Analyze single phase and three phase AC circuits.

CO2: Demonstrate their understanding about earthing and different types of wiring.

CO3: Demonstrate their understanding about different types of measuring instruments and their usage.

CO4: Identify and analyse the parts of DC machines, Transformers, alternators and Induction machines.

CO5: To get an overview of special electrical machines.

Note: I) PART - A is compulsory. Two marks for each question.II) PART - B: Answer any Two sub questions (from a, b, c) for a Maximum of 18 marks from each unit.

| Q. No. | Questions | Marks |
|----------------------|---|-----------|
| I : PART - A | | 10 |
| I a. | Define form factor and obtain the value of it for an AC quantity. | 2 |
| b. | What is phase sequence? Explain the same with the help of relevant figure. | 2 |
| c. | Bring out the difference between statically induced emf and dynamically induced emf. | 2 |
| d. | Define the terms; | 2 |
| | i) Self-inductance and ii) Mutual inductance, giving the expression for each. | 2 |
| e. | Mention any four applications of a permanent magnet stepper motor. | 2 |
| II : PART - B | | 90 |
| UNIT - I | | 18 |
| 1 a. | Starting with the methods of generation of sinusoidal ac voltages, obtain the expression for alternating emf. With the help of figure. | 9 |
| b. | With relevant circuit diagram and phasor diagram prove that the average power consumed by a pure capacitor is zero. | 9 |
| c. | A choke coil takes a current of 2 A, lagging 60° behind the applied voltage of 200 V at 50 Hz, Calculate the inductance, resistance and impedance of the coil. Also determine the power consumed when it is connected across 100 V, 25 Hz supply. | 9 |
| UNIT - II | | 18 |
| 2 a. | A balanced 3- ϕ , y connected load of 150 kW takes a leading current of 100 A with a line voltage of 1100 V, 50 Hz. Find the circuit constants of load per phase. | 9 |
| b. | With neat circuit diagram, derive the relationship for voltages and currents in star connected system. | 9 |
| c. | What is electric shock? State the causes and precautions to be taken to prevent it. | 9 |

UNIT - III**18**

- 3 a. What is DC generator? Explain with the help of connection diagram and important relations, the various classifications of DC generators. 9
- b. A 4 pole lap wound shunt generator delivers 200 amperes at terminal voltage of 250 volts, It has a armature and field resistance of 0.05Ω and 50Ω , respectively. Neglecting the brush drop, Determine; 9
- i) Armature current ii) The current per armature parallel path
iii) EMF generated iv) Power developed
- c. Bring out the difference between synchronous generator and DC generator. Derive the emf equation of synchronous generator. With suitable notations. 9

UNIT - IV**18**

- 4 a. What is transformer? Discuss the various types of losses occurring in a transformer and hence, obtain the expression for efficiency of transformer. 9
- b. A 600 kVA, 1- ϕ transformer has an efficiency of 92% both at full load and half load at unity power factor. Determine its efficiency at 75% of full load at 0.9 power factor lag. 9
- c. State the advantages and disadvantages of 3- ϕ , IM (induction motor).what is slip? Obtain the expression for slip and give its significance. 9

UNIT - V**18**

- 5 a. What is the difference between brushless DC motor and normal DC motor. Explain with help of neat sketch the construction and working of brushless DC motor. 9
- b. What is stepper motor? Explain the construction and working of permanent magnet stepper motor. 9
- c. What is servomotor? With neat diagram, explain the working principle of the same. 9

* * * *