



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
Third Semester, B.E. - Electronics and Communication Engineering
Semester End Examination; March / April - 2022
Network Analysis and Synthesis

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1: Ability to apply the fundamental concepts in solving and analyzing different Electrical networks.

CO2: Ability to solve circuits using appropriate technique.

CO3: Ability to apply mathematics in analyzing and synthesizing the networks in time and frequency domain.

CO4: Ability to analyze the performance of a particular network.

CO5: Ability to formulate various synthesis methods for different one-port networks.

Note: I) PART - A is compulsory. Two marks for each question.

II) PART - B: Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

| Q. No. | Questions | Marks | BLs | COs | POs |
|----------------------|---|-----------|-----|-----|-------|
| I : PART - A | | 10 | | | |
| I a. | State Super-Position theorem. | 2 | L1 | CO1 | PO1,2 |
| b. | Define Bandwidth and Selectivity of a series RLC circuit. | 2 | L1 | CO1 | PO1,2 |
| c. | State Initial value theorem. | 2 | L1 | CO1 | PO1,2 |
| d. | Draw the dual of the network shown. | 2 | L1 | CO1 | PO1,2 |
| e. | State Hurwitz Polynomial. | 2 | L2 | CO1 | PO1,2 |
| II : PART - B | | 90 | | | |
| UNIT - I | | 18 | | | |

1 a. Find V_a , V_b and V_c using node analysis in the circuit shown in Fig.1.

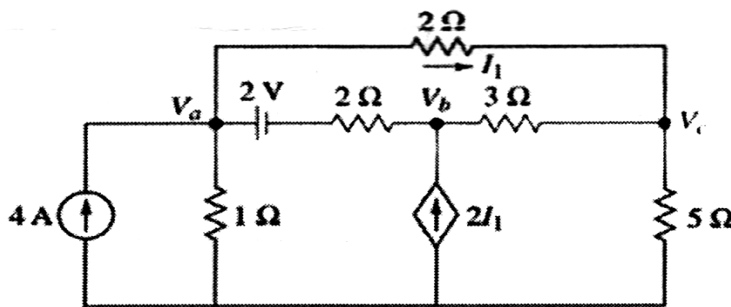


Fig.1

9 L3 CO2 PO2,3

b. Using source transformation, find the power delivered by the 50 V source for the circuit shown in Fig. 2


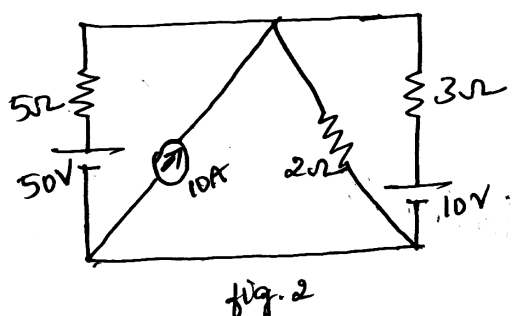


fig. 2

9 L3 CO2 PO2,3

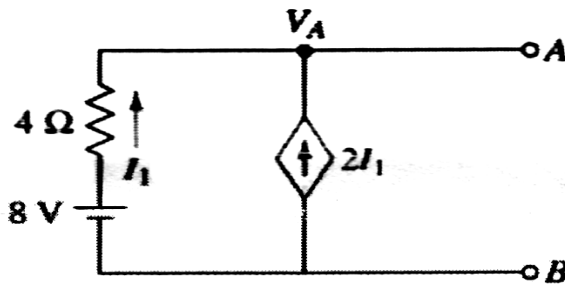- c. Obtain the Thevenin's equivalent network for the network shown in Fig.3 at terminal A and B.



9 L3 CO3 PO3,4

Fig.3


UNIT - II

18

- 2 a. What is Resonance? Show that resonant frequency of series resonance circuit is equal to the geometric mean of two half power frequencies.

9 L1 CO1 PO1,2

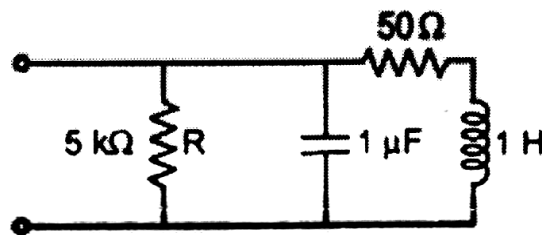
- b. For the network shown in Fig. 4, determine;
 i) Resonant frequency ii) Input admittance iii) Quality Factor
 iv) BW v) Half Power frequencies



9 L3 CO4 PO2

Fig.4.

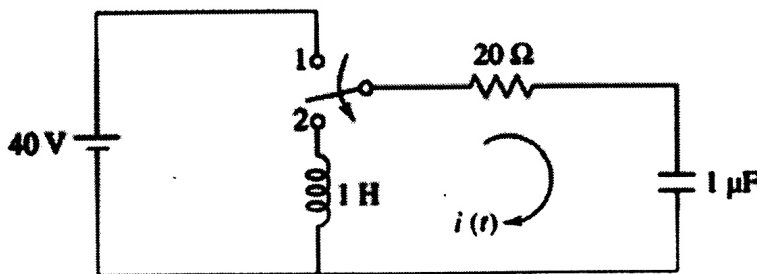- c. In the network shown in the Fig. 5, the switch is changed from the position 1 to position 2 at $t = 0$, steady condition having reached before switching. Find the values of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0+$



9 L3 CO3 PO3,4

Fig.5

UNIT - III

18

- 3 a. Find the inverse Laplace transform of $F(s) = \frac{s^2 + 3}{(s^2 + 2s + 5)(s + 2)}$.

9 L3 CO3 PO2,4

- b. The network shown in Fig. 6 was in steady state before $t = 0$. The switch is opened at $t > 0$. Find $i(t)$ for $t > 0$ using Laplace transform.

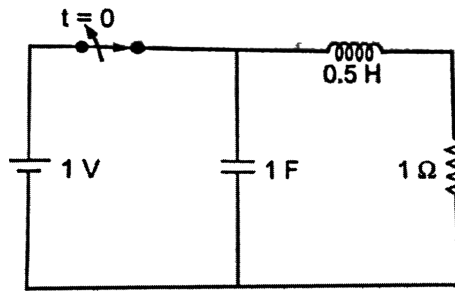


Fig.6

9 L3 CO4 PO2,4

- c. Find the Laplace transform of,

i) $f(t) = t e^{-at}$

ii) $f(t) = t e^{-at} \cos \omega t$

iii) $f(t) = \sinh(\omega t)$

9 L3 CO3 PO2,4

UNIT - IV

18

- 4 a. Find the H parameter for the two port network shown in the following Fig. 7.

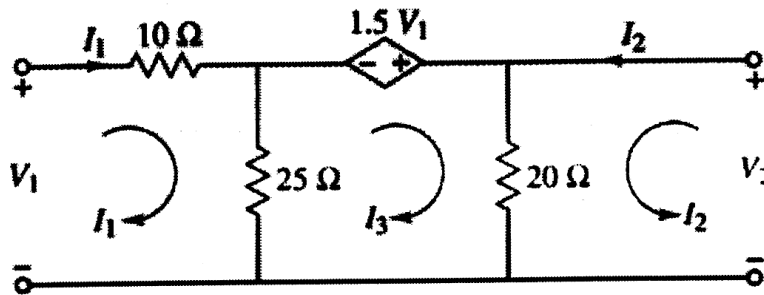


Fig.7

9 L3 CO5 PO3

- b. Explain the following terms:

- i) Duality ii) Tree iii) Oriented graph
- iv) Branch v) Link vi) Rank of graph

9 L3 CO5 PO3

- c. For the network shown in Fig. 8, write down the F-cutset matrix and obtain the network equilibrium equation on node basis and calculate 'v'.

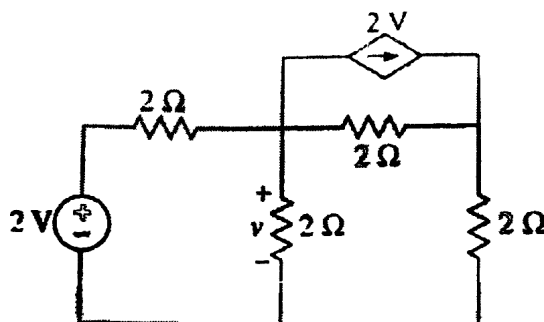


Fig. 8

9 L3 CO5 PO3

UNIT - V

18

5 a. Test whether $F(s) = \frac{s^2+1}{s^3+4s}$ is positive real function.

9 L3 CO5 PO3

b. Realize the foster form-I for the following RC impedance function:

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

9 L3 CO5 PO3

c. Realize the faster form-II for the following LC impedance function:

$$Z(s) = \frac{(s+1)(s+4)}{(s+5)(s+3)}$$

9 L3 CO5 PO3

* * *