



**P.E.S. College of Engineering, Mandya - 571 401**  
 (An Autonomous Institution affiliated to VTU, Belagavi)  
**Third Semester, B.E. - Electrical and Electronics Engineering**  
**Semester End Examination; March / April - 2022**  
**Electrical Circuit Analysis**

Time: 3 hrs

Max. Marks: 100

*Course Outcomes*

The Students will be able to:


- CO1: To solve problems on electrical network using different techniques and theorems, resonance concepts.
- CO2: To obtain graphical solution to electrical networks using Network Topology.
- CO3: Analyze the network under transient condition due to switching.
- CO4: Analyze and obtain the time domain response of R, L, C circuits for all types of excitations using Laplace transforms.
- CO5: Represent the two port networks by Z, Y, ABCD and Parameters and Assessment of stability of network from network function.

**Note:** I) PART - A is compulsory. Two marks for each question.

II) PART - B: Answer any Two sub questions (from a, b, c) for Maximum of 18 marks from each unit.

Q. No.	Questions	Marks
<b>I : PART - A</b>		<b>10</b>
I a.	Write the circuit symbols for four dependent sources.	2
b.	Mention any two dirichlet conditions of Fourier series.	2
c.	Obtain the Laplace transform of a Gate function.	2
d.	Three similar resistors are connected in star across 450 V, 3 phase lines. The line current is 10 A. If the same resistors are connected in delta across the same supply, calculate the power consumed.	2
e.	List any four properties of driving point admittance of LC network.	2
<b>II : PART - B</b>		<b>90</b>
<b>UNIT - I</b>		<b>18</b>

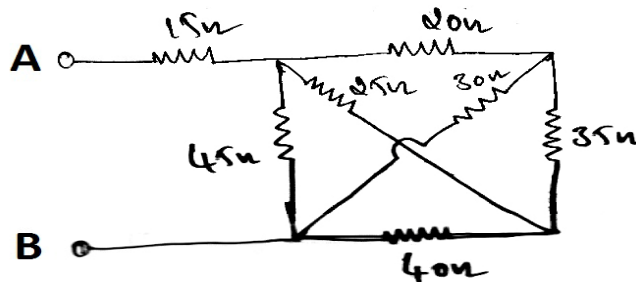1 a. Find an equivalent resistance between A and B for the network shown below,



9

b. Solve for the current  $I$  in the circuit shown in Fig. Q1(b) using node analysis.


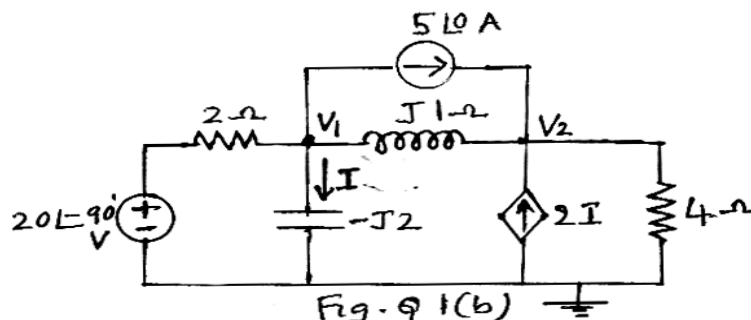


Fig. Q 1(b)

9

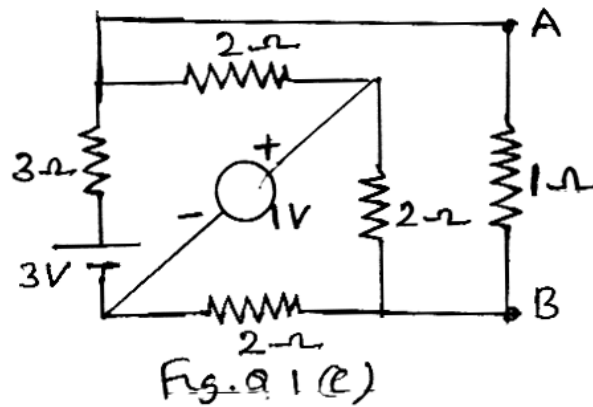- c. Find the Thevenins equivalent circuit at the terminals AB for the network shown in Fig.Q1(c) and hence determine the current in the resistance of  $1 \Omega$  connected between AB.




9

UNIT - II

18

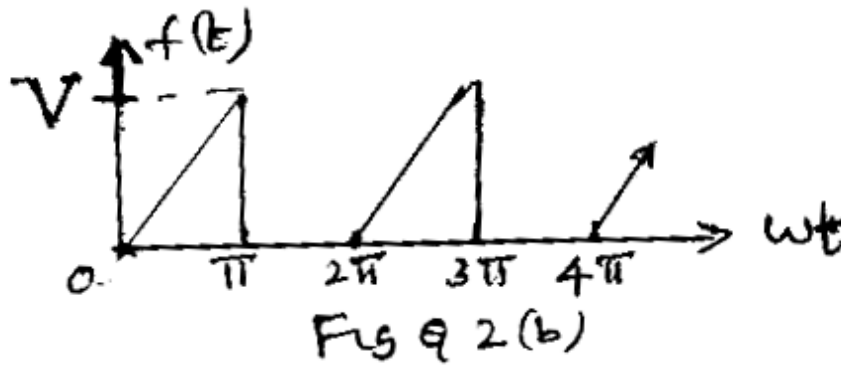- 2 a. List the properties of series resonance and give the applications of the same.  
 b. Find the trigonometric Fourier series for the waveform shown in Fig. Q2(b).



9


- c. A voltage  $v = 50 + 25 \sin 500t + 10 \sin 1500t + 5 \sin 2500t$  volts applied to the terminals of a passive network and the resulting current is,  
 $i = 5 + 2.23 \sin(500t - 26.6^\circ) + 0.556 \sin(1500t - 56.3^\circ) + 0.186 \sin(2500t - 68.2^\circ)$  A.  
 Find the effective voltage, effective current and the average power.

9

UNIT - III


18

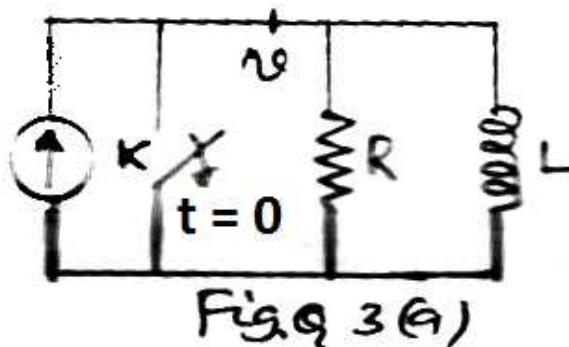- 3 a. In the given network of Fig. Q3(a), the switch 'K' is opened at  $t = 0$ . At  $t = 0+$  solve for the values of  $v$ ,  $\frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$  if  $I = 2$  A,  $R = 200 \Omega$  and  $L = 1$  H.



9

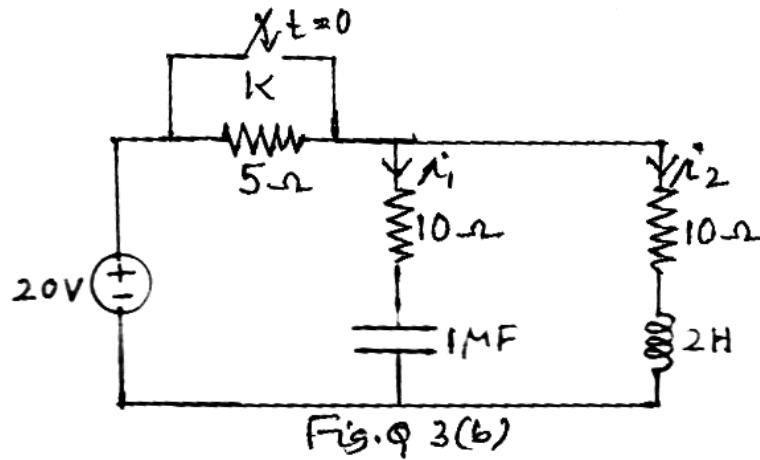
- b. In the circuit shown in Fig. Q3(b), steady state is reached with switch 'K' open. The switch is closed at  $t = 0$ . Determine  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  at  $t = 0+$ .



9

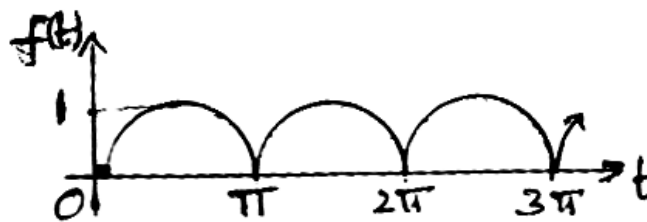- c. For the waveform shown below, show that the Laplace transform is given by

$$F(s) = \frac{1}{(s^2 + 1)} \coth\left(\frac{\pi s}{2}\right).$$



9


UNIT - IV

18

- 4 a. A three phase, three wire, 100 volts, ABC system supplies a balanced delta connected load with impedances of  $20\angle 45^\circ$  ohms. Determine the line current and draw the phasor diagram.
- b. (i) Obtain Z-parameters in terms of y-parameters.
- (ii) Find Z-parameters for the network shown in Fig. 4b.


9

4

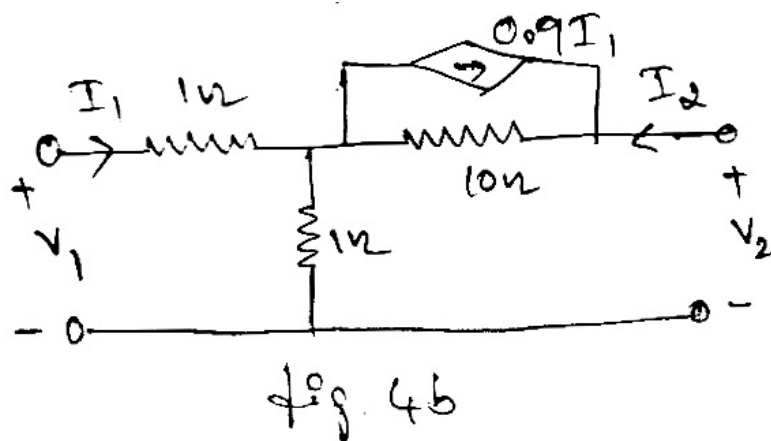

5

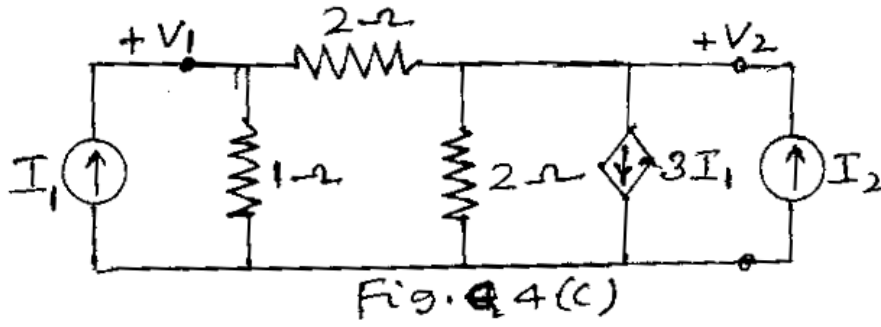c. Find the 'h' parameters of the network shown in Fig. Q4(c).




9

UNIT - V

18

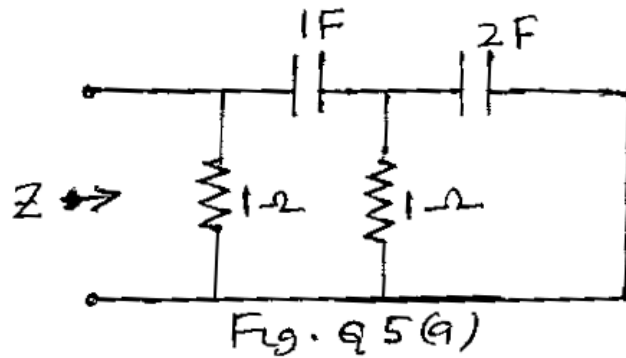5 a. Find the transform impedance of the network shown in Fig. Q5(a).




9

b. Explain significance of poles and zeroes and draw pole-zero plot for,

$$V(S) = \frac{(S+1)(S+3)}{(S+2)(S+4)}$$

9

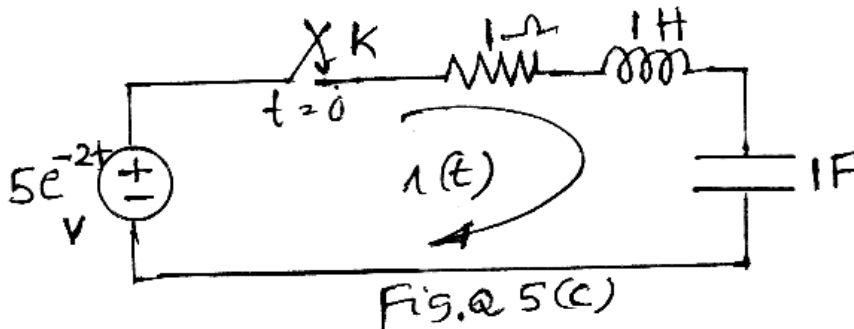c. In the network shown in Fig. Q5(c), the switch 'K' is closed at  $t = 0$ . Find an expression for the current  $i(t)$  using Laplace transform method.



9

\*\*\*