



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Fifth Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; February / March - 2022

Power Electronics

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1: Select various types of power semiconductor devices to develop different types of Power converter systems based on control characteristics.

CO2: Analyze the different base drive control methodologies and various types of Protection Circuits needed for converter system.

CO3: Distinguish between various types of power converter systems, compare and analyze them.

CO4: Understand and analyze the various types of commutation circuits and implement them.

CO5: Design and develop different types of converter and inverter system.

Note: I) PART - A is compulsory. Two marks for each question.

II) PART - B: Answer any **Two** sub questions (from a, b, c) for Maximum of **18 marks** from each unit.

| Q. No. | Questions | Marks | BLs | COs | POs |
|----------------------|--|-----------|-----|-----|-----|
| I : PART - A | | 10 | | | |
| I a. | Differentiate between diode and SCR. | 2 | L3 | CO1 | PO1 |
| b. | What are the peripheral effects in power electronics equipments? | 2 | L1 | CO2 | PO1 |
| c. | What do you mean by phase angle control? | 2 | L1 | CO3 | PO1 |
| d. | Define duty ratio of a chopper. | 2 | L1 | CO4 | PO1 |
| e. | What is the function of freewheeling diode? | 2 | L1 | CO5 | PO1 |
| II : PART - B | | 90 | | | |
| UNIT - I | | 18 | | | |
| 1 a. | List the various applications of power electronics converters. | 9 | L1 | CO1 | PO1 |
| b. | Sketch and explain the switching characteristics of IGBT. | 9 | L2 | CO1 | PO1 |
| c. | Explain the control characteristics of SCR and MOSFET device. | 9 | L2 | CO1 | PO1 |
| UNIT - II | | 18 | | | |
| 2 a. | Explain the two transistor model of a thyristor and show that anode current is affected by gate current. | 9 | L4 | CO2 | PO2 |
| b. | Explain dynamic turn-on and turn-off characteristics of a SCR. | 9 | L4 | CO2 | PO2 |
| c. | Explain; | 9 | L2 | CO2 | PO2 |
| | i) Need of snubber circuit ii) dv/dt and di/dt protection | | | | |
| UNIT - III | | 18 | | | |
| 3 a. | With circuit diagram and waveform, explain the working of a single phase bi-directional AC voltage controller for inductive load. Derive the RMS output voltage. | 9 | L2 | CO3 | PO2 |
| b. | What is commutation? With diagram and waveform, explain working of an impulse resonant commutation. | 9 | L2 | CO3 | PO1 |

- c. An AC voltage controller has a resistive load $R = 10 \Omega$, RMS input voltage $V_s = 120 \text{ V}$, at 60 Hz . The thyristors is ON for $n = 25$ cycles and is off for $m = 75$ cycles. Determine;
- 9 L2 CO3 PO2
- i) RMS output voltage (V_o)
- ii) Input PF
- iii) Avg. and RMS current in thyristors

UNIT - IV**18**

- 4 a. With circuit diagram and waveform, explain the chopper classification and their applications. 9 L2 CO4 PO1
- b. With necessary circuit and waveforms, explain three phase bridge inverter in 120° mode. 9 L4 CO4 PO1
- c. A chopper is supplied to inductive load with a freewheeling diode. $L = 5 \text{ H}$, $R = 10 \Omega$. The input to the chopper is 200 V and the chopper frequency is 100 Hz . The ON to OFF time ratio is 2:3. Compute; 9 L2 CO4 PO2
- i) Average load current
- ii) Limits between which current fluctuates

UNIT - V**18**

- 5 a. Explain the principle operation of 3- ϕ half wave converter with R-load. Derive an expression for its output voltage of RMS value. 9 L4 CO5 PO1
- b. i) List the comparison of half controlled and fully controlled rectifiers. 6
- ii) Explain the performance parameters of a line commutated converters. 3
- L2 CO5 PO1
- c. Explain the principle of operation of 1- ϕ full wave converter with RL load. Derive an expression for its out voltage of Avg and RMS values. 9 L4 CO5 PO2

* * * *