

**P.E.S. College of Engineering, Mandya - 571 401***(An Autonomous Institution affiliated to VTU, Belagavi)***Third Semester, B.E. - Information Science and Engineering****Semester End Examination; March / April - 2022****Digital Design**

Time: 3 hrs

Max. Marks: 100

Course Outcomes*The Students will be able to:**CO1: Apply the principles of Boolean algebra/K - Map to manipulate and minimize logic expressions/functions.**CO2: Analyze and design Arithmetic Circuits and Data processing Circuits.**CO3: Design different units that are elements of typical computer's CPU using VHDL.**CO4: Design logic circuits using flip-flops/latches/registers.**CO5: Analyze and design Asynchronous and Synchronous Sequential circuits.***Note: I) PART - A is compulsory. Two marks for each question.****II) PART - B: Answer any Two sub questions (from a, b, c) for Maximum of 18 marks from each unit.**

Q. No.	Questions	Marks	BLs	COs	POs
I : PART - A		10			
I a.	Draw the logic circuit for the Boolean expression $Y = AB' + A'B$.	2	L1	CO1	PO1
b.	Draw the truth table for 2:4 decoder.	2	L1	CO2	PO1
c.	Write the excitation table of JK flip flop.	2	L1	CO3	PO1
d.	Write the truth table of 4-bit Johnson counter	2	L1	CO4	PO1
e.	Write the state diagram of D flip flop.	2	L1	CO5	PO1
II : PART - B		90			
UNIT - I		18			
1 a.	Perform the following operations (show the step by step calculation)				
	i) $(0.8125)_{10} = ()_2$				
	ii) $(29.45)_{10} = ()_8$	9	L3	CO1	PO1
	iii) $(0.A38)_{16} = ()_2$				
b.	i) Draw the AND, OR, NOT gates using NAND gates.				
	ii) Simplify the expression using K-Map method,	9	L3	CO1	PO1
	$F = (A, B, C, D) = \sum m(3, 5, 12, 13) + d(7, 8, 10, 11)$				
c.	Write the truth table and logic circuits for the following Boolean expression:				
	i) $F = (A+B) + C$				
	ii) $F = (A+B).C'$	9	L3	CO1	PO2
	iii) $F = AB' + AC$				
	iv) $F = (A'+B)(A+B')$				
	v) $F = (A+B)'.C$				
UNIT - II		18			
2 a.	Simplify the following function using Quine-Meccusky method,				
	$F(A, B, C, D) = \sum(2, 6, 8, 9, 10, 11, 14, 15)$.	9	L3	CO2	PO2
b.	Define decoders. Explain 2:4 decoder using logic gates and design a Full adder circuit using decoder IC.	9	L2	CO2	PO1

- c. Define Multiplexer. Explain 4 to 1 multiplexer with neat circuit diagram. Implement Boolean function $F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$ using multiplexer.

9 L2 CO2 PO1

UNIT - III

18

- 3 a. Explain a 4-bit carry look-ahead adder.
- b. Explain clocked SR flip flop and JK flip flop with neat circuit diagram and timing diagram.
- c. Derive the characteristic equation, draw state transition diagram and excitation table of the D and T flip flops. Implement SR flip flop using JK flip flop.

9 L2 CO3 PO1

9 L2 CO3 PO1

9 L2 CO3 PO1

UNIT - IV

18

- 4 a. Explain ring counter and johnson counter in detail.
- b. Design an asynchronous decade counter and explain with timing diagram.
- c. Design mod-5 synchronous counter using JK flip flop and implement the same.

9 L1 CO4 PO1

9 L2 CO4 PO1


9 L2 CO4 PO1

UNIT - V

18


- 5 a. Design a simple detector circuit for the sequence 011 using Moore model.
- b. Reduce state transition diagram (Moore model) of Fig. 5(b) by row elimination method and implication table method.

9 L2 CO5 PO1

 

9 L2 CO5 PO1

 - c. Analyse the Melay model asynchronous sequential circuit of Fig. 5(c) and show its stable state and corresponding outputs and also give the state diagram of this circuit.



9 L3 CO5 PO1