



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Second Semester, B.E. - Semester End Examination; October - 2022

Basic Electrical Engineering

(Common to All Branches)

Time: 3 hrs

Max. Marks: 100

Course Outcomes

The Students will be able to:

CO1: Analysis of single phase AC circuits.

CO2: Illustrate the working DC Machine as a Generator and Motor.

CO3: Analyze the three phase AC circuits and explain the working of three phase induction motor.


CO4: Discuss the working of transformer and alternator.

CO5: Describe the concept of green energy and basics of power systems.

Note: I) PART - A is compulsory. Two marks for each question.

II) PART - B: Answer any Two sub questions (from a, b, c) for a Maximum of 18 marks from each unit.

Q. No.	Questions	Marks	BLs	COs
I : PART - A		10		
1 a.	Calculate the power consumed by a single phase AC circuit having 55 kVA apparent power and a power factor of 0.85.	2	L1	CO1
b.	Write the emf equation of a DC generator and mention the parameters in the equation.	2	L1	CO2
c.	Calculate the rotor current frequency in an Induction motor, if the supply is 50 Hz and slip is 3%.	2	L1	CO3
d.	The primary current of a transformer is 25 A and the transformation ratio is 0.6. Determine the secondary current.	2	L1	CO4
e.	Define renewable energy sources.	2	L1	CO5
II : PART - B		90		
UNIT - I		18		
2 a.	i) Explain the significance of power factor in an AC circuit.	3	L1	CO1
	ii) Determine the current through a series circuit having 20 Ω resistance in series with a capacitor of 16.67 μF and an inductance of 0.5 H. Also determine the power factor of the circuit. Assume a supply of 110 V, 50 Hz across the RLC series combination.	6	L1	CO1
b.	Give a detailed analysis of RL series circuit supplied by an AC source, with relevant waveforms and phasor diagram.	9	L1	CO1
c.	Determine the branch currents and main current in the following circuit			
	Q2(c). What is the equivalent impedance between points A and B.			

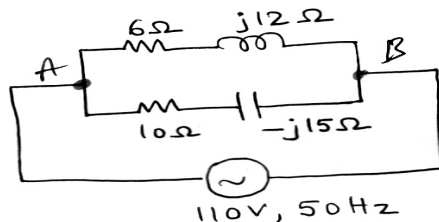

Circuit Q2(c)

UNIT - II**18**

- 3 a. Explain the construction of DC machines with neat sketch. 9 L1 CO2
- b. i) What is back emf? Explain the significance. 3 L1 CO2
- ii) A four pole, lap wound DC shunt generator has a useful flux per pole of 0.08 wb. The armature winding consists of 260 turns, each of resistance 0.006 Ω . Determine the terminal voltage of the generator when it is running at 1000 rpm and supplying a load current of 55 A. 6 L1 CO2
- c. i) Mention the application of DC series motor and DC shunt motor. 3 L2 CO2
- ii) An 8 pole DC shunt generator has 778 wave connected conductors on its armature. While running at 500 rpm it supplies power to a load of 12.5 Ω at 250 V. The armature and shunt field resistances are 0.24 Ω and 250 Ω respectively. Determine the armature current the emf induced and the flux per pole. 6 L2 CO2

UNIT - III**18**

- 4 a. i) Derive relation between line and phase quantities in a delta connected system. 6 L1 CO3
- ii) Three equal impedances (10+j16) Ω are connected in star across a 400 V, 60 Hz supply. Determine the total power consumed by the load. 3 L1 CO3
- b. Three coils having impedances of (8+j6) Ω are connected;
- i) Star ii) Delta, across a 440 V, 50 Hz 3 phase line. Calculate line current and total power consumed in each case. 9 L2 CO3
- c. I) Explain the construction of;
- i) Slip ring rotor 6 L2 CO3
- ii) Squirrel cage rotor of an induction motor
- II) A 6 pole induction motor is fed from 50 Hz supply. If the frequency of rotor emf at full load is 2 Hz, find the full load slip and speed. 3 L2 CO3

UNIT - IV**18**

- 5 a. i) Derive the emf equation of an alternator. 6 L2 CO4
- ii) Compare the salient and non-salient rotors of an alternator. 3 L2 CO4
- b. I) Derive the emf equation of a single phase transformer. 5 L1 CO4
- II) A 25 kVA transformer has 500 turns on the primary and 40 turns on the secondary winding the primary winding is connected to a 3 kV, 50 Hz AC sources calculate;
- i) Primary and secondary current on full load 4 L1 CO4
- ii) The maximum flux in the core

- c. I) Write a note on the losses in a transformer. 3 L1 CO4
- II) A single phase 50 Hz transformer has 30 primary and 350 secondary turns the net cross sectional area of the core is 250 cm². If the primary winding is connected to a 230 V, 50 Hz supply, calculate; 6 L1 CO4
- i) The peak value of the flux density in the core
- ii) Voltage induced in the secondary winding
- iii) Primary current when secondary current is 100 A

UNIT - V**18**

- 6 a. With a neat diagram, explain the working of wind power plant. 9 L1 CO5
- b. i) What are circuit breakers? Give its classification. 4 L1 CO5
- ii) Explain the construction and operation of HRC fuse. 5 L1 CO5
- c. With a neat sketch, explain the pipe earthing system. 9 L2 CO5

* * * *