

U.S.N 

--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

**First / Second Semester, B.E. - Semester End Examination; August - 2023**

### Basic Electronics

(Common to All Branches)

Time: 3 hrs

Max. Marks: 100

#### Course Outcomes

The Students will be able to:

CO1: Apply knowledge of physics and mathematics to understand operation of PN diodes, Zener diodes, MOSFET, solar cells, LCD, CRT, Transducers, modulation techniques and Opamps.

CO2: Analyse circuits built with diodes, Zener diodes, MOSFET and Opamp

CO3: Design simple circuit to perform rectification, voltage regulation, Opamp based amplifier, summer and filter.

CO4: Analyse and implement basic Digital Electronic circuits for a given application using knowledge of Boolean Algebra and Basic gates.

CO5: Discuss different modulation techniques and communication systems.

**Note: I) PART - A is compulsory. Two marks for each question.**

**II) PART - B: Answer any Two sub questions (from a, b, c) for a Maximum of 18 marks from each unit.**

Q. No.	Questions	Marks	BLs	COs	POs
<b>I : PART - A</b>		<b>10</b>			
1 a.	Draw the block diagram of power supply unit.	2	L1	CO1	PO1
b.	List any two differences between Depletion type and Enhancement type MOSFET.	2	L1	CO1	PO1
c.	List the ideal characteristics of Op-amp.	2	L1	CO1	PO1
d.	Write the 1's and 2's complement of binary number 1101011010.	2	L2	CO4	PO2
e.	Define amplitude modulation and draw modulated signal.	2	L1	CO5	PO2
<b>II : PART - B</b>		<b>90</b>			
<b>UNIT - I</b>		<b>18</b>			
2 a.	Determine $V_{DQ}$ and $I_{DQ}$ for the series diode configuration circuit with input 10 V, consisting of Silicon diode and resistor of 2 K $\Omega$ .	9	L3	CO3	PO2
b.	Explain the working of Full wave Bridge Rectifier with the help of circuit diagram and waveforms.	9	L2	CO1	PO1
c.	Explain the working of Zener diode as voltage regulator for the condition of fixed $V_i$ and variable $R_L$ with necessary diagram and equations.	9	L2	CO1	PO1
<b>UNIT - II</b>		<b>18</b>			
3 a.	Explain the Construction, Operation and Characteristics of $n$ -channel Depletion-type MOSFET with necessary diagrams.	9	L2	CO1	PO1
b.	Explain the construction and operation of CMOS inverter.	9	L3	CO3	PO2
c.	Draw the Enhancement-type MOSFET amplifier using voltage divider configuration. Sketch its corresponding ac equivalent circuit.	9	L2	CO2	PO1

Find the equations for the following:

- i)  $g_m$  and  $g_{m0}$
- ii)  $Z_i$  and  $Z_o$
- iii)  $A_v$

**UNIT - III**

**18**

- 4 a. Derive an expression for voltage gain ( $A_v$ ) of an inverting Op-Amp with the help of circuit diagram and its ac equivalent circuit. 9 L2 CO2 PO2
- b. Explain the following with necessary diagram and equations:
  - i) Op-Amp as an Integrator 9 L2 CO2 PO2
  - ii) Op-Amp Summing Amplifier
  - iii) Op-amp first order Low pass filter
- c. Explain the following controlled sources with required ideal diagram and circuit diagram: 9 L3 CO3 PO3
  - i) Voltage Controlled Voltage Source
  - ii) Voltage Controlled Current Source

**UNIT - IV**

**18**

- 5 a. Compute the following:
  - i)  $(1234.12)_{10} = ( )_2 = ( )_8 = ( )_{16}$  9 L2 CO4 PO3
  - ii) Binary Multiplication  $(1011)_2 * (101)_2$
  - iii) Perform binary subtraction using 2's complement  $(15)_{10} - (3)_{10}$
- b. Design and implement the full adder using 2-half adder with characteristics equation for sum and carry. 9 L4 CO4 PO2
- c. Implement the following logic gates using only NAND and NOR
  - i) AND 9 L2 CO4 PO3
  - ii) OR
  - iii) XOR

**UNIT - V**

**18**

- 6 a. Explain Amplitude Modulation (AM) with waveforms and equation along with spectrum diagram of AM wave. 9 L2 CO5 PO2
- b. Explain super heterodyne receiver used in radio receivers with neat block diagram. 9 L2 CO5 PO2
- c. Explain the advantages and application of Optical fiber communication. 9 L2 CO5 PO2