



--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. - Computer Science and Engineering

### Logic Design

Time: 3 hrs

Max. Marks: 100

Note: Answer any FIVE full questions, selecting at least TWO full questions from each part.

#### PART - A

- 1.a What are universal gates? Realize basic gates using any one of the universal gate. 8
- b. Convert the given expression in standard SOP forms; 8
- i)  $f(A, B, C) = A + AB + CB$       ii)  $f(P, Q, R) = PQ + R + PR$
- c. Simplify the following Boolean equation using Boolean laws. 4
- $Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}C + ABC$
- 2.a Reduce the following function using K-map technique and implement using gates. 10
- i)  $f(P, Q, R, S) = \sum m(0, 1, 4, 8, 9, 10) + d(2, 11)$
- ii)  $f(A, B, C, D) = \prod M(0, 2, 4, 10, 11, 14, 15)$
- b. Simplify the following Boolean function by using QM method 10
- $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$
- 3.a Implement the following Boolean function using 8x1 MUX 10
- $F(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$
- b. What is carry look ahead adder? Design 2-bit carry look ahead adder. 10
- 4.a Give the characteristic equation, state diagram and excitation table of SR, JK and T flip flop 9
- b. Convert SR flip flop to JK flip flop 6
- c. Explain Master slave JK flip flop. 5

#### PART - B

- 5.a Explain serial in serial out and parallel in serial out register with a neat Logic diagram 10
- b. Explain the working of Johnson counter and Ring counter 10
- 6.a Design a synchronous mod-3 counter with the following sequence using clocked JK flip flops 10
- count sequence  $\rightarrow 0, 1, 2, 0, 1, 2, \dots$
- b. Draw and explain the working of 4 bit up/down synchronous counter. 10
- 7.a Explain state reduction technique with a neat diagram. 10
- b. Distinguish between Mealy model and Moore model. 10
- 8.a Explain dual slope A/D conversion with a neat diagram. 10
- b. Explain R-2R ladder D to A conversion. 10