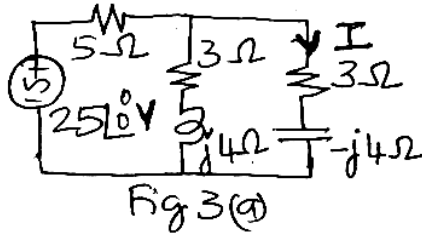


UNIT - II


- 3 a. Verify reciprocity theorem for the network shown in Fig. 3(a).



6


- b. A series RLC circuit is excited by a constant voltage variable frequency supply. Draw the variations of all relevant variables as a function of frequency.
- c. Find using the Norton's equivalent network, the current in the Resistor R for the network shown in Fig. 3(c)

6

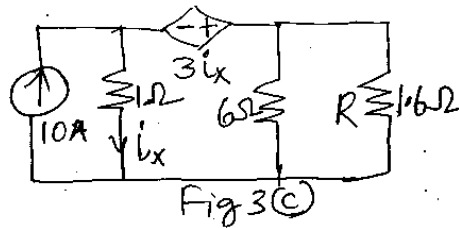


8

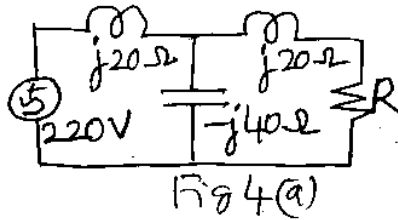- 4 a. Find the value of R in the network shown in Fig. 4(a) which receives maximum power from the source. Find this maximum power.



6

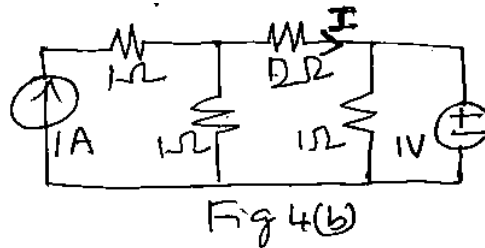- b. Find I in the network shown in Fig. 4(b) using superposition principle.



6

- c. A resistance of 1 Ω, a capacitor of 0.5 F and a coil of 1 Ω resistance and inductance of 1 H are all connected in parallel to a supply. Find the resonant frequency and admittance at resonance.


8

UNIT - III

- 5 a. Show that the locus of the current in a series RL circuit is circular.


6

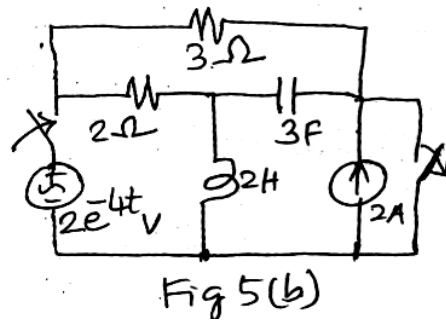- b. Draw the dual of the network shown in Fig. 5(b). Write the corresponding equations for the two networks.



6

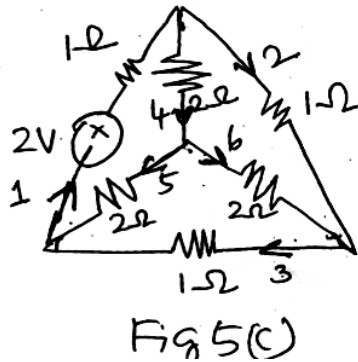- c. Draw the graph of the network shown in Fig. 5(C), select the tree as 4, 5, 6. Find basic cutset matrix. There from, find basic loop matrix.



8

- 6 a. What are dual elements and dual networks? List the dual elements. Give the stepwise procedure to draw a dual network. 6
- b. For the network graph of the network shown in Fig. 5(c) and for the specified tree, obtain the loop equations. 6
- c. Consider a parallel circuit with $Z_1 = R_1 + jX_L$ and $Z_2 = R_2 - jX_c$. If each one of these four elements is varied one at a time, draw the total current locus in each case. 8

UNIT - IV

- 7 a. Explain phase sequence, positive sequence and negative sequence of a three phase system. Draw a 3 - wire and 4 - wire three phase system. Establish the relation between line and phase voltages in a star connection. 10
- b. A balanced 3-ph, 440 V, RYB sequence supply feeds an unbalanced star load. When the phase R supply voltage is $254\angle -30^\circ V$, the voltage across the phase R impedance load is $200\angle -15^\circ V$. Find the voltage in the other load phase. 10
- 8 a. The phase current I_{AB} of a balanced delta connected load fed by a 3-phase 220 V, ABC sequence supply is $10\angle -30^\circ A$. Find the line currents. Draw the complete phasor diagram. Find the total power consumed by the load and the resistive part of the load. 10

- b. Three impedances $Z_A = 50\angle 0^\circ$, $Z_B = j10\ \Omega$, $Z_C = -j10\ \Omega$ are star connected across a 3 phase, 100 V, ABC sequence supply. Find neutral shift voltage and all the load phase voltages. 10

UNIT - V

- 9 a. What are the conditions for the existence of FS representation? Give the three forms of the FS expansion of a periodic signal. 8
- b. Find the exponential Fourier series of a saw tooth wave form of amplitude A, period of 2π , starting from 0. 12
- 10 a. Discuss the various symmetries in the FS analysis. 8
- b. A series RL circuit with $R = 18\ \Omega$, and $L = 0.0413\ \text{H}$ is fed from a source of $v(t)$ given by $v(t) = 180\sin(314t + 10^\circ) + 56\sin(942t + 35^\circ) + 18\ \text{V}$ Find;
- i) The expression for current 12
- ii) rms value of $v(t)$ and $i(t)$
- iii) pf of the circuit.

* * * *