



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec. - 2015

Analog Electronics Circuit

Time: 3 hrs

Max. Marks: 100

Note: Answer *FIVE* full questions, selecting *ONE* full question from each *unit*.

UNIT - I

- 1 a. With circuit diagram and related waveform, explain the working principle of voltage doubler circuit. 6
- b. How clamping circuits differ from clipping circuit? With neat circuit diagram, explain negative clamper. 8
- c. For the circuit shown in Fig. 1. (c) using silicon transistor with $V_{BE} = 0.7 \text{ V}$ and $\beta = 80$ find, 6
 i) All resistance values ii) V_{CE} , given $V_C = 7.6 \text{ V}$, $V_E = 2.4 \text{ V}$ and $I_C = 2 \text{ mA}$.
- 2 a. With circuit diagram, input – output waveform and transfer characteristics explain Double – ended clipper. 7
- b. For the zener diode network shown in Fig. 2(b), determine V_L , V_R , I_Z and P_Z . 6
- c. For a voltage divider bias circuit, derive an expression for I_B , I_C and V_{CE} . 7

UNIT - II

- 3 a. For the collector feedback bias circuit, derive an expression for $S(I_{CO})$ and $S(V_{BE})$. 7
- b. For a common base amplifier using transistor with the following hybrid parameters, 6
 $h_{ib} = 22 \Omega$, $h_{fb} = -0.98$, $h_{rb} = 26 \times 10^{-4}$, $h_{ob} = \frac{1}{2} \text{ M}\Omega$, find;
 i) Current gain ii) Input impedance iii) Voltage gain
 iv) Output impedance v) Voltage gain considering source.
- c. Applying dual of Miller's theorem find R_i and R_{ix} for the circuit shown using transistor Fig. 3(c). 7
 $h_{ie} = 1 \text{ k}$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = \frac{1}{40} \text{ k}$
- 4 a. What is BIAS compensation? With circuit, explain diode compensation for V_{BE} . 6
- b. Explain Millers Theorem and its Dual. 8
- c. For a CE Amplifier configuration Hybrid model Derive an expression for, 6
 i) Current gain ii) Input impedance iii) Voltage gain.

UNIT - III

- 5 a. Derive an expression for low frequency response of an amplifier, plot magnitude and phase characteristics. 10
- b. Explain Voltage – series feedback Amplifier and Voltage shunt feedback amplifier. 10
- 6 a. Explain the RC coupled amplifier circuit and its frequency response. 8
- b. List the advantages of Negative feedback. 4
- c. Explain effect of negative feedback on output resistance of a voltage series feedback amplifier. 8

UNIT - IV

- 7 a. Classify and explain power amplifiers in details. 8
- b. The class A 4 transformer coupled audio power amplifier is required to deliver a maximum of 1 W into a loud speaker of $10\ \Omega$ resistances. If the output resistance of the amplifier is $1000\ \Omega$ calculate; 4
- i) Turns ratio of the transformer required.
- ii) Power supply voltage, Assume an ideal transformer.
- c. For a class B push – pull power amplifier with $V_{CC} = 25\ \text{V}$ driving a $8\ \Omega$ load find, 8
- i) Maximum input power ii) Maximum output power
- iii) Maximum circuit efficiency iv) Maximum collection dissipation.
- 8 a. A transformer – coupled Class – A amplifier drives a $16\ \Omega$ loud speaker through a 4:1 transformer. With $V_{cc} = 36\ \text{V}$, the circuit delivers 2 W to the load find. (Assume 100% efficiency of transformer), 10
- i) Power across the transformer primary ii) rms voltage across the load
- iii) rms voltage across transformer primary iv) rms value of load current
- v) Conversion efficiency if the dc collection current is 150 mA.
- b. Explain working of class B push pull amplifier and show that the conversion efficiency is 78.54%. 10

UNIT - V

- 9 a. Explain oscillator working principle and state Barkhausen's criteria for sustained oscillations. 7
- b. Explain E – MOSFET characteristics. 7
- c. A Hartley oscillator uses a transistor with $h_{fe} = 40$, find the value of L_1 , L_2 and C for a frequency of oscillation of 60 kHz. 6
- 10 a. Explain RC phase shift oscillator? State conditions for sustained oscillations. 7
- b. Explain D – MOSFET characteristics. 6
- c. Explain the working of crystal oscillator? What is piezoelectric effect? 7

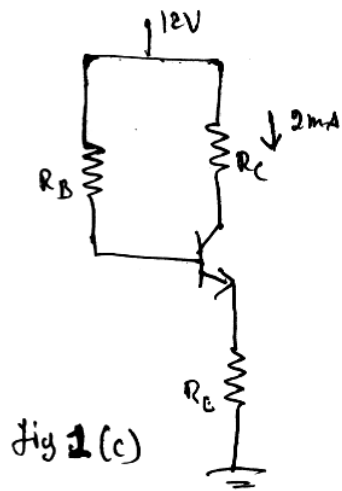


Fig 1(c)

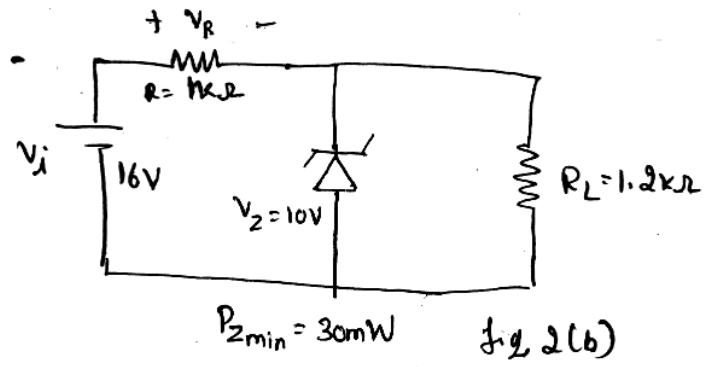


Fig 2(b)

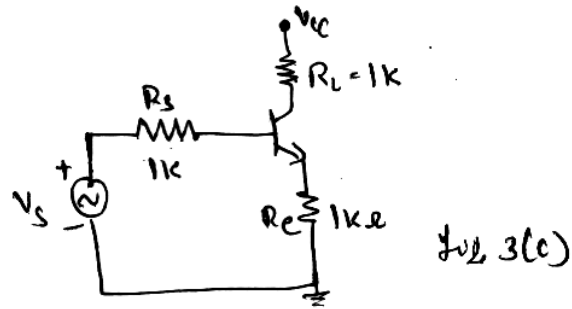


Fig 3(c)
