



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec. – 2015

Digital Electronics


Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions selecting **ONE** full question from each **unit**.
ii) Assume suitable missing data if any.

UNIT - I

- 1 a. Mention the advantages of digital systems over analog systems. 5
- b. Construct the truth table for each of the following Boolean functions 10
 - i) $f(x, y, z) = yz + (\bar{x} + y)(\bar{x} + \bar{z})$ ii) $f(w, x, y, z) = wxy + \bar{w}(\bar{y} + z)$
- c. Complement the following Boolean expressions, 5
 - i) $y = \bar{a}\bar{b}(ab + b\bar{d})$ ii) $y = \bar{a}\bar{b}(ab)$
- 2 a. State and prove Redundant Literal Rule (RLR) using relevant truth table. 6
- b. Show that $y = f(A, B, C) = \sum(0, 1, 3, 4, 6, 7)$ is the complement of $y = f(A, B, C) = \pi(2, 5)$ 8
- c. Draw the simplest possible logic diagram that implements the output of the logic diagram shown below

 

UNIT - II

- 3 a. Minimize and implement the following multiple output. Functions in SOP form using K-Map 10
 - i) $F = \sum m(1, 2, 5, 6, 8, 9, 10)$ ii) $F = \sum m(0, 1, 4, 6, 8, 9, 11) + d(2, 7, 13)$
- b. Find a minimal sum for the Boolean function using Quine McClusky method and PI table reduction $F(a, b, c, d, e) = \sum m(0, 1, 9, 15, 24, 29, 30) + d(8, 11, 31)$ 10
- 4 a. Realize full subtractor using only NOR gates. 8
- b. Design a 4 – bit carry look ahead adder and write the logic circuit. 8
- c. Draw the circuit of full adder using two half adders. 4

UNIT - III

- 5 a. Define encoder. Explain Decimal to BCD encoder with logic symbol, truth table and circuit diagram. 7
- b. Implement the following function using a decoder minimizing the number of inputs to be summed, 5


$$f_1(a,b,c) = \sum m(0,2,3,5,6,7) \qquad f_2(a,b,c) = \sum m(1,3,4,6,7)$$
- c. Define demultiplexer and design 1:8 line DE – MUX with an illustrative truth table and circuit involving basic gates. 8
- 6. a. With the help of logic diagram and truth table explain DF/F and S. R F/F. 8
- b. Distinguish between combinational and sequential circuits. 4
- c. Explain the working of Master slave JK flip flop with logic diagram. 8

UNIT - IV

- 7 a. Explain Mealy and Moore Models of a clocked sequential circuit. 10
- b. Design a 3 – bit synchronous up counter using JK flip – flops. 10
- 8 a. With a neat logic diagram, explain the working of a 4 – bit PISO register. 10
- b. Distinguish between synchronous and asynchronous counter. 4
- c. Explain the operation of 4 – bit Johnson counter with the help of logic diagram and state diagram. 6

UNIT - V

 - 9 a. Explain the operation of 4 – bit binary weighted DAC and also derive the expression for a output voltage. 10
- b. Determine the output voltage of the circuit as shown in Fig. Q. (b) when digital inputs are 0010 and 1010.



- c. Explain the operation of flash ADC. 5
- 10 a Define the following terms: 8
 - i) Fan out ii) Noise Margins iii) Propagation delay iv) Power dissipations
- b. Explain briefly Emitter Coupled Logic (ECL) with circuit diagram. 6
- c. Draw and explain MOS inverter circuits. 6